

ELECTRIC CIRCUITS


EXERCISES

Section 25.1 Circuits, Symbols, and Electromotive Force

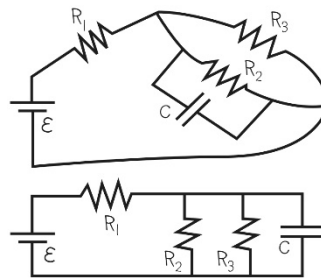- 11. INTERPRET** This problem is an exercise in drawing a circuit diagram, given a written description of the circuit in terms of its capacitors, resistors, and battery.

DEVELOP A literal reading of the circuit specifications results in connections like those in sketch (a), below.

EVALUATE See sketch below. Because the connecting wires are assumed to have no resistance (a real wire is represented by a separate resistor), a topologically equivalent circuit diagram is shown in sketch (b).




ASSESS There are three paths to ground (or to the negative battery terminal), two of which go through resistors and the third of which goes through the capacitor.

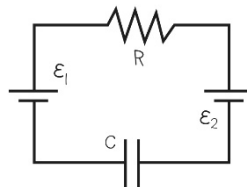- 12. INTERPRET** This problem involves connecting the various given circuit elements in series to form a closed circuit.

DEVELOP In a series circuit, the same current must flow through all elements. The order of the elements is not specified, so we can connect them in any order we like, provided that they are connected in series.

EVALUATE One possibility is shown below. The order of elements and the polarity of the battery connections are not specified.




ASSESS An important feature about a series circuit is that the current through all the components must be the same. With two batteries, the direction of the current flow is determined by the polarity of the battery with the larger voltage.

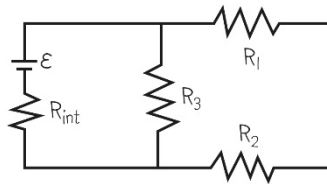- 13. INTERPRET** This problem involves drawing a circuit diagram from the description given in the problem statement.

DEVELOP The circuit has three parallel branches: one with R_1 and R_2 in series; one with just R_3 ; and one with the battery.

EVALUATE See the figure below. R_{int} is the internal resistance of the battery.



ASSESS This circuit has no capacitors, so we could replace R_1 , R_2 , and R_3 by an equivalent resistance

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_3} + \frac{1}{R_1 + R_2}$$

$$R_{\text{eq}} = \frac{R_3(R_1 + R_2)}{R_3 + R_2 + R_1}$$

- 14. INTERPRET** This problem explores the connection between the emf of a battery and the energy it delivers. We are to find the emf of a battery given the work it does to move a given amount of charge.

DEVELOP Electromotive force, or emf, is defined as work per unit charge, $\mathcal{E} = W/q$ (see discussion accompanying Fig. 25.2).

EVALUATE Substituting the values given in the problem statement, the emf is

$$\mathcal{E} = \frac{W}{q} = \frac{27 \text{ J}}{3.0 \text{ C}} = 9.0 \text{ V}$$

ASSESS For an ideal battery with zero internal resistance, the emf is equal to the terminal voltage (potential difference across the battery terminals).

- 15. INTERPRET** This problem involves finding out for how long a battery can supply the given current while maintaining its rated voltage. We are given the total energy stored in the battery; so, if we can find the power the battery must deliver, we can find the time needed to deplete this energy reservoir.

DEVELOP Delivering the given current at the rated voltage results in a power expenditure of

$$\bar{P} = IV$$

(see Equation 24.7). Because the average power is defined as $\bar{P} = \Delta W / \Delta t$, we can find Δt , given that the energy we have to spend is $\Delta W = 5.0 \text{ kJ}$.

EVALUATE Solving for the time interval Δt and inserting the known quantities gives

$$\Delta t = \frac{\Delta W}{\bar{P}} = \frac{\Delta W}{IV} = \frac{5.0 \text{ kJ}}{(1.5 \text{ V})(0.60 \text{ A})} = 5.6 \times 10^3 \text{ s} = 1.5 \text{ h}$$

ASSESS This result assumes that the battery voltage does not decrease as it depletes its store of energy, which is not a realistic assumption (although for most batteries, the departure from the ideal situation assumed in this problem is not huge).

- 16. INTERPRET** This problem involves finding the (chemical) energy consumed in the battery for the work done.

DEVELOP The power delivered by an emf is $P = IV$ (see Equation 24.7). Therefore, if the voltage and current remain constant, then the energy consumed is $W = Pt = IVt$.

EVALUATE Substituting the values given, the energy used in

$$W = IVt = (5 \text{ A})(12 \text{ V})(3600 \text{ s}) = 200 \text{ kJ}$$

to a single significant figure.

ASSESS The result makes sense; the energy used up is proportional to the current drawn, the emf (i.e., voltage), and the time during which the headlights were left on.

Section 25.2 Series and Parallel Circuits

17. INTERPRET This problem involves calculating the equivalent resistance of the given resistor combination.

DEVELOP Apply Equations 25.1 and 25.3b. For the parallel pair of resistors R_1 and R_2 , Equation 25.3b gives

$$R_{1,2} = \frac{R_1 R_2}{R_1 + R_2}$$

Combining this in series with resistor R_3 (via Equation 25.1) gives

$$R_{1,2,3} = R_3 + R_{1,2} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

EVALUATE Inserting the given resistances gives

$$R_{1,2,3} = 22 \text{ k}\Omega + \frac{(49 \text{ k}\Omega)(39 \text{ k}\Omega)}{49 \text{ k}\Omega + 39 \text{ k}\Omega} = 44 \text{ k}\Omega$$

ASSESS The final resistance is greater than the resistance of R_3 alone, as expected, but it is less than the resistance of R_1 alone. This is because R_2 is parallel to R_1 and allows some current to flow through the circuit without traversing R_1 (i.e., it adds another “traffic lane”).

18. INTERPRET This problem is about connecting two resistors in parallel and calculating the equivalent resistance.

DEVELOP The equivalent resistance of two resistors connected in parallel can be found by Equation 25.3a:

$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

The equation allows us to determine R_2 when R_{parallel} and R_1 are known.

EVALUATE The solution for R_2 in Equation 25.3a is

$$R_2 = \frac{R_1 R_{\text{parallel}}}{R_1 - R_{\text{parallel}}} = \frac{(65 \text{ k}\Omega)(54 \text{ k}\Omega)}{65 \text{ k}\Omega - 54 \text{ k}\Omega} = 320 \text{ k}\Omega$$

to two significant figures.

ASSESS Our result shows that $R_2 > R_{\text{parallel}}$. This is consistent with the fact that the equivalent resistance R_{parallel} is smaller than R_1 and R_2 because each individual resistor reduces the resistance of the parallel resistor circuit because they add new “traffic lanes” that allow charge to move through the circuit more easily.

19. INTERPRET This problem involves analyzing a real battery circuit. We are given the rated voltage of the battery and its real voltage when it powers the defective starter and are asked to find its real voltage for a proper starter.

DEVELOP This problem is similar to Example 25.2, which shows that the battery is connected in series with the load (i.e., the starter motor, which we treat as a resistor). To find the internal resistance of the battery, we use the macroscopic version of Ohm’s law, $V = IR$:

$$V_{\text{terminals}} = 7.33 \text{ V} = \mathcal{E} - IR_{\text{int}} = 12.6 \text{ V} - (285 \text{ A})R_{\text{int}}$$

$$R_{\text{int}} = 0.0185 \Omega$$

where $V_{\text{terminals}}$ is the actual voltage across the battery’s terminals. Knowing the internal resistance of the battery, we can repeat this calculation to find $V_{\text{terminals}}$ when a proper starter is used.

EVALUATE The voltage across the terminals when a proper starter is used is

$$V_{\text{terminals}} = 12.6 \text{ V} - (112 \text{ A})(0.0185 \Omega) = 10.5 \text{ V}$$

ASSESS Because the battery has an internal resistance, the voltage it can deliver is reduced by the voltage drop across the internal battery.

20. INTERPRET This problem is about the internal resistance of the battery in Problem 25.19.

DEVELOP The starter circuit contains all the resistances in series, as in Fig. 25.9. (We assume R_L includes the resistance of the cables, connections, etc., as well as that of the motor.) With the defective starter, the terminal voltage is

$$V_{\text{term}} = \mathcal{E} - IR_{\text{int}}$$

$$7.33 \text{ V} = 12.6 \text{ V} - (285 \text{ A})R_{\text{int}}$$

EVALUATE From the equation above, we find the internal resistance to be

$$R_{\text{int}} = \frac{\mathcal{E} - V_{\text{term}}}{I} = \frac{(12.6 \text{ V} - 7.33 \text{ V})}{285 \text{ A}} = 0.0185 \Omega$$

ASSESS The terminal voltage $V_{\text{term}} = 7.33 \text{ V}$ is substantially less than the battery's emf $\mathcal{E} = 12.6 \text{ V}$. The two are equal only in the ideal case where the internal resistance vanishes.

21. INTERPRET We are to find the internal resistance of a battery, given its short-circuit current and its rated voltage.

DEVELOP The battery contains an internal resistance (see section "Real Batteries"), which we can find using the macroscopic version of Ohm's law, $V = IR$, where $V = \mathcal{E} = 9\text{V}$.

EVALUATE Inserting the given quantities into Ohm's law gives

$$R_{\text{int}} = \mathcal{E} / I = (9 \text{ V}) / (0.38 \text{ A}) = 24 \Omega$$

ASSESS This is a rather large value for an internal resistance of a 9-V battery.

22. INTERPRET In this problem we are asked to find all possible values of equivalent resistance that could be obtained with three resistors.

DEVELOP Since each resistor can be placed either in parallel or in series, there are eight combinations using all three resistors. To find the equivalent resistance, use Equations 25.1 and 25.3a.

EVALUATE Let $R_1 = 1.0 \Omega$, $R_2 = 2.0 \Omega$, and $R_3 = 3.0 \Omega$. The possible results are (a) one resistor in series with two resistors in parallel

$$R_3 + \frac{R_1 R_2}{R_1 + R_2} = 3.0 \Omega + \frac{(1.0 \Omega)(2.0 \Omega)}{1.0 \Omega + 2.0 \Omega} = \frac{11}{3} \Omega = 3.7 \Omega$$

$$R_2 + \frac{R_1 R_3}{R_1 + R_3} = 2.0 \Omega + \frac{(1.0 \Omega)(3.0 \Omega)}{1.0 \Omega + 3.0 \Omega} = \frac{11}{4} \Omega = 2.8 \Omega$$

$$R_1 + \frac{R_2 R_3}{R_2 + R_3} = 1.0 \Omega + \frac{(2.0 \Omega)(3.0 \Omega)}{2.0 \Omega + 3.0 \Omega} = \frac{11}{5} \Omega = 2.2 \Omega$$

(b) one in parallel with two in series:

$$\frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3} = \frac{(3.0 \Omega)(1.0 \Omega + 2.0 \Omega)}{1.0 \Omega + 2.0 \Omega + 3.0 \Omega} = \frac{9}{6} \Omega = 1.5 \Omega$$

$$\frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3} = \frac{(2.0 \Omega)(1.0 \Omega + 3.0 \Omega)}{1.0 \Omega + 2.0 \Omega + 3.0 \Omega} = \frac{8}{6} \Omega = 1.3 \Omega$$

$$\frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3} = \frac{(1.0 \Omega)(2.0 \Omega + 3.0 \Omega)}{1.0 \Omega + 2.0 \Omega + 3.0 \Omega} = \frac{5}{6} \Omega = 0.83 \Omega$$

(c) three in series: $R_1 + R_2 + R_3 = 1.0 \Omega + 2.0 \Omega + 3.0 \Omega = 6.0 \Omega$.

(d) three in parallel:

$$\left(R_1^{-1} + R_2^{-1} + R_3^{-1} \right)^{-1} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{(1.0 \Omega)(2.0 \Omega)(3.0 \Omega)}{(1.0 \Omega)(2.0 \Omega) + (1.0 \Omega)(3.0 \Omega) + (2.0 \Omega)(3.0 \Omega)} = \frac{6}{11} \Omega = 0.55 \Omega$$

ASSESS The equivalent resistance is a maximum when all three are connected in series, as in (c), and a minimum when all are connected in parallel, as in (d).

Section 25.3 Kirchhoff's Laws and Multiloop Circuits

23. INTERPRET This problem requires us to find the currents in all parts of a multiloop circuit.

DEVELOP The general solution of the two loop equations and one node equation given in Example 25.4 can be found using determinants (or I_1 and I_2 can be found in terms of I_3 , as in Example 25.4). The equations and the solution are:

$$I_1 R_1 + 0 + I_3 R_3 = \mathcal{E}_1 \quad (\text{loop 1})$$

$$0 - I_2 R_2 + I_3 R_3 = \mathcal{E}_2 \quad (\text{loop 2})$$

$$I_1 - I_2 - I_3 = 0 \quad (\text{node A})$$

$$\Delta \equiv \begin{vmatrix} R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \\ 1 & -1 & -1 \end{vmatrix} = R_1 R_2 + R_2 R_3 + R_3 R_1, \quad I_1 = \frac{1}{\Delta} \begin{vmatrix} \varepsilon_1 & 0 & R_3 \\ \varepsilon_2 & -R_2 & R_3 \\ 0 & -1 & -1 \end{vmatrix} = \frac{\varepsilon_1(R_2 + R_3) - \varepsilon_2 R_3}{\Delta}$$

$$I_2 = \frac{1}{\Delta} \begin{vmatrix} R_1 & \varepsilon_1 & R_3 \\ 0 & \varepsilon_2 & R_3 \\ 1 & 0 & -1 \end{vmatrix} = \frac{\varepsilon_1 R_3 - \varepsilon_2(R_1 + R_3)}{\Delta}, \quad I_3 = \frac{1}{\Delta} \begin{vmatrix} R_1 & 0 & \varepsilon_1 \\ 0 & -R_2 & \varepsilon_2 \\ 1 & -1 & 0 \end{vmatrix} = \frac{\varepsilon_2 R_1 + \varepsilon_1 R_2}{\Delta}$$

EVALUATE With the particular values of emfs and resistors in this problem, we have

$$\Delta = R_1 R_2 + R_2 R_3 + R_3 R_1 = (2 \, \Omega)(4 \, \Omega) + (4 \, \Omega)(1 \, \Omega) + (1 \, \Omega)(2 \, \Omega) = 14 \, \Omega^2$$

and the currents are

$$I_1 = [(R_2 + R_3)\varepsilon_1 - R_3\varepsilon_2]\Delta^{-1} = \frac{(4 \, \Omega + 1 \, \Omega)(6 \, \text{V}) - (1 \, \Omega)(1.1 \, \text{V})}{14 \, \Omega^2} = 2.06 \, \text{A} = 2.1 \, \text{A}$$

$$I_2 = [R_3\varepsilon_1 - (R_1 + R_3)\varepsilon_2]\Delta^{-1} = \frac{(1 \, \Omega)(6 \, \text{V}) - (2 \, \Omega + 1 \, \Omega)(1.1 \, \text{V})}{14 \, \Omega^2} = 0.193 \, \text{A} = 0.19 \, \text{A}$$

$$I_3 = (R_2\varepsilon_1 + R_1\varepsilon_2)\Delta^{-1} = \frac{(4 \, \Omega)(6 \, \text{V}) + (2 \, \Omega)(1.1 \, \text{V})}{14 \, \Omega^2} = 1.87 \, \text{A} = 1.9 \, \text{A}$$

to a single significant figure.

ASSESS The same results could be obtained by retracing the reasoning of Example 25.4, with $\varepsilon_2 = 1.1 \, \text{V}$ replacing the original value in loop 2. Then, everything is the same until the equation for loop 2: $1.1 + 4I_2 - I_3 = 0$.

- 24. INTERPRET** This problem asks us to find the current through a resistor in a circuit.

DEVELOP The right-hand side of this circuit is irrelevant for this problem because the emf source is directly connected to the resistor without any intervening resistances, so the voltage drop across the resistor is simply the emf voltage. Thus, we can apply the macroscopic version of Ohm's law to find the current.

EVALUATE The current is $I_{3\Omega} = V_{3\Omega}/R_{3\Omega} = (6 \, \text{V})/(3 \, \Omega) = 2 \, \text{A}$.

ASSESS Note that if the 6-V battery had an internal resistance, an argument like that used in Example 25.4 must be applied.

- 25. INTERPRET** We are to find the current through a resistor in a given circuit, for which we can use Kirchhoff's laws. We will use the loops and nodes drawn in Example 25.4.

DEVELOP The circuit is given to us in Fig. 25.14, with one change: $\varepsilon_2 = 2.0 \, \text{V}$. We will use node A and loops 1 and 2. These will give us three equations, which we will use to solve the three unknown currents. At node A, $-I_1 + I_2 + I_3 = 0$. For loop 1, $\varepsilon_1 - I_1 R_1 - I_3 R_3 = 0$. For loop 2, $\varepsilon_2 + I_2 R_2 - I_3 R_3 = 0$.

EVALUATE Because we are interested in the current I_2 , we eliminate the other two currents. The node equation gives us $I_1 = I_2 + I_3$. Substitute this into the equation for loop 1 and solve for I_3

$$\varepsilon_1 - (I_2 + I_3)R_1 - I_3 R_3 = 0$$

$$I_3 = \frac{\varepsilon_1 - I_2 R_1}{R_1 + R_3}$$

Now substitute this value into the equation for loop 2 and solve for I_2 :

$$\varepsilon_2 + I_2 R_2 - \frac{\varepsilon_1 - I_2 R_1}{R_1 + R_3} R_3 = 0$$

$$\varepsilon_2(R_1 + R_3) + I_2 R_2(R_1 + R_3) - \varepsilon_1 R_3 + I_2 R_1 R_3 = 0$$

$$\varepsilon_2(R_1 + R_3) + I_2(R_1 R_2 + R_2 R_3 + R_1 R_3) - \varepsilon_1 R_3 = 0$$

$$I_2 = \frac{\varepsilon_1 R_3 - \varepsilon_2(R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_1 R_3} = \frac{(6 \, \text{V})(1 \, \Omega) - (2 \, \text{V})(3 \, \Omega)}{8 \, \Omega^2 + 4 \, \Omega^2 + 2 \, \Omega^2} = 0 \, \text{V}/\Omega = 0 \, \text{A}$$

ASSESS The current through resistor R_2 is zero! Looking back at the original diagram, we can see that this would mean that battery 2 is supplying no current and the voltage drops through resistors 1 and 3 equal the voltage supplied by battery 1. This is a somewhat unexpected solution, but it is consistent.

Section 25.4 Electrical Measurements

- 26. INTERPRET** This problem requires us to determine the error in a voltage measurement that results from the internal resistance of the voltmeter.

DEVELOP The voltage across the 10-k Ω resistor in Fig. 25.27 is $(150 \text{ V})(10)/(10+5)=100 \text{ V}$ (the circuit is just a voltage divider, as described by Equations 25.2a and 25.2b), as would be measured by an ideal voltmeter with infinite resistance. With the real voltmeter connected in parallel across the 10-k Ω resistor, the effective resistance is changed to $R_{||} = (10 \text{ k}\Omega)(280 \text{ k}\Omega)/(290 \text{ k}\Omega) = 9.66 \text{ k}\Omega$, so we can find the measurement-error ratio.

EVALUATE The measured voltage is

$$\frac{(150 \text{ V})(9.66)}{9.66 + 5} = 98.8 \text{ V}$$

which is about 1.2% lower than the true voltage.

ASSESS The measured voltage is slightly lower than the real voltage because the voltmeter allows some of the current to bleed through it, thus reducing the current that has to traverse the 10-k Ω resistor.

- 27. INTERPRET** This problem involves finding the measurement error caused by the nonzero resistance of the ammeter used to measure the current.

DEVELOP The current in the circuit of Fig. 25.27 is

$$I = \frac{V}{R_{\text{tot}}} = \frac{V}{R_1 + R_2} = \frac{150 \text{ V}}{5 \text{ k}\Omega + 10 \text{ k}\Omega} = 10 \text{ mA}$$

With the ammeter inserted (in series with the resistors), the resistance R_{tot} is increased by $R_A = 100 \Omega$.

EVALUATE The resulting current after including R_A is

$$I' = \frac{V}{R_1 + R_2 + R_A} = \frac{150 \text{ V}}{5 \text{ k}\Omega + 10 \text{ k}\Omega + 0.10 \text{ k}\Omega} = 9.93 \text{ mA}$$

which is about 0.66% lower than I .

ASSESS The current reading by the ammeter is lower due to its internal resistance.

- 28. INTERPRET** We are to find the power dissipated in a circuit where the given voltage is discharged through the resistance that is the series resistance of the internal resistances of the battery and the ammeter.

DEVELOP The series resistance through which the voltage is discharged is

$$R_{\text{series}} = R_{\text{bat}} + R_{\text{meter}}$$

The current flowing through this circuit is $I = V / R_{\text{tot}} = V / (R_{\text{bat}} + R_{\text{meter}})$, and the power dissipated in the meter is (Equation 24.8a) $P = I^2 R_{\text{meter}}$.

EVALUATE Inserting the given values, the power dissipated is

$$P = I^2 R_{\text{meter}} = \frac{\mathcal{E}^2 R_{\text{meter}}}{(R_{\text{bat}} + R_{\text{meter}})^2} = \frac{(12 \text{ V})^2 (0.3 \Omega)}{(0.31 \Omega)^2} = 0.45 \text{ kW}$$

ASSESS This power is comparable to that consumed by a small toaster oven. The ammeter would be destroyed quickly.

Section 25.5 Capacitors in Circuits

- 29. INTERPRET** In this problem we are asked to show that the quantity RC , the product of resistance and capacitance, has units of time.

DEVELOP The SI units for R and C are Ω and F, respectively. The units can be rewritten as

$$1 \Omega = 1 \frac{\text{V}}{\text{A}} = 1 \frac{\text{V}}{\text{C/s}} = 1 \frac{\text{V} \cdot \text{s}}{\text{C}}, \quad 1 \text{ F} = 1 \frac{\text{C}}{\text{V}}$$

EVALUATE From the expressions above, the SI units for the time constant, RC , are

$$\Omega \cdot \text{F} = \left(\frac{\text{V} \cdot \text{s}}{\text{C}} \right) \left(\frac{\text{C}}{\text{V}} \right) = \text{s}$$

as stated.

ASSESS The quantity RC is the characteristic time for changes to occur in an RC circuit.

- 30. INTERPRET** This problem requires us to find the time units for the RC time constant when the resistance R is given in various units.

DEVELOP From the results of the previous problem, we know that an $\Omega \cdot \text{F} = \text{s}$, so any prefactors applied to Ω or F are simply applied to s .

EVALUATE (a) $(\Omega)(\mu\text{F}) = \mu\text{s}$, (b) $(\text{k}\Omega)(\mu\text{F}) = 10^3 \times 10^{-6} \text{ s} = \text{ms}$, (c) $(\text{M}\Omega)(\mu\text{F}) = 10^6 \times 10^{-6} \text{ s} = \text{s}$.

ASSESS The prefactors μ , M , k , and so on are simply multiples of 10, so they can be treated mathematically as for scalar factor.

- 31. INTERPRET** This problem involves the time dependence of the capacitor voltage in a charging RC circuit. We are to find the charging ratio of a capacitor after 5 RC time constants.

DEVELOP The capacitor voltage as a function of time is given by Equation 25.6:

$$V_{\text{cap}} = \mathcal{E}(1 - e^{-t/RC})$$

EVALUATE When $t = 5RC$, the equation above gives a voltage of

$$\frac{V_{\text{cap}}}{\mathcal{E}} = 1 - e^{-5} = 1 - 6.74 \times 10^{-3} \approx 99.3\%$$

of the applied voltage.

ASSESS As time goes on and after many more time constants, we find essentially no current flowing to the capacitor, and the capacitor could be considered as being fully charged for all practical purposes.

- 32. INTERPRET** This problem involves an RC circuit. We are to find the time required for the capacitor to charge, given the voltage, resistance, and capacitance of the circuit.

DEVELOP The capacitor voltage as a function of time is given by Equation 25.6:

$$V_{\text{cap}} = \mathcal{E}(1 - e^{-t/RC})$$

EVALUATE Solving the expression above for time and inserting the given quantities gives

$$t = RC \ln \left(\frac{\mathcal{E}}{\mathcal{E} - V_C} \right) = (10 \mu\text{F})(470 \text{ k}\Omega) \ln \left(\frac{250}{250 \text{ V} - 140 \text{ V}} \right) = 3.86 \text{ s}$$

ASSESS Because the circuit capacitance takes time to discharge, this explains why, to start afresh, we need to turn devices such as computers off for several seconds before turning them back on.

- 33. INTERPRET** We are to find the voltage across the capacitor in Fig. 25.23a when it is fully charged, which implies that the current through the capacitor is zero.

DEVELOP Use the results of Example 25.6 and Ohm's law to find the voltage required. If the capacitor is fully charged, then no current flows through it and the circuit is equivalent to the circuit shown in 25.23c. So we find the current through resistor R_2 in Fig. 25.23c and then determine the voltage across resistor R_2 , which will be the same as the voltage across the capacitor.

EVALUATE The current through resistor R_2 is given in Example 25.6 as $I = \mathcal{E}/(R_1 + R_2)$. The voltage is given by Ohm's law as

$$V = IR = \left(\frac{\mathcal{E}}{R_1 + R_2} \right) R_2 = \mathcal{E} \left(\frac{R_2}{R_1 + R_2} \right)$$

ASSESS In the limit of long charging times, this circuit behaves like a voltage divider.

EXAMPLE VARIATIONS

- 34. INTERPRET** This problem asks for the current in one resistor that's part of a more complex circuit. So, it's about analyzing a circuit with series and parallel components.

DEVELOP Approaching this problem like the original example, we will follow the steps in Tactics 25.1, but will replace the $4.0\text{-}\Omega$ resistor with a $2.0\text{-}\Omega$ resistor. This means that the equivalent resistance obtained from the two $2.0\text{-}\Omega$ resistor in parallel becomes: $R_{\text{parallel}} = (2\Omega)(2\Omega)/(2\Omega + 2\Omega) = 1\Omega$. Adding the remaining three resistances in series results in: $R_{\text{series}} = 1\Omega + 1\Omega + 3\Omega = 5\Omega$. To obtain the current which flows through these three resistances, and in particular the $2.0\text{-}\Omega$ resistor, we apply Ohm's law.

EVALUATE From Ohm's law we find: $I_{5\Omega} = 12\text{V}/5\Omega = 2.4\text{A}$. Since this current flows across the equivalent resistance R_{parallel} made up of two identical $2.0\text{-}\Omega$ resistors, half of that current will flow through each one, making the current through the resistor $I_{2\Omega} = 1.2\text{A}$.

ASSESS Note how, in solving this problem, we used Ohm's law to find, alternately, voltage and then current in different resistances. We also find that this current is smaller since the $2.0\text{-}\Omega$ resistor is now connected in parallel with a resistance which is smaller than in the original example.

- 35. INTERPRET** This problem asks for the possible voltage across a circuit, if the power dissipated across one resistor is known. So, it's about analyzing a circuit with series and parallel components.

DEVELOP Approaching this problem like the original example, we will follow the steps in Tactics 25.1, but will treat the voltage as V unknown. This means that the equivalent resistance obtained from the two resistors in parallel is again: $R_{\text{parallel}} = (2\Omega)(4\Omega)/(2\Omega + 4\Omega) = 1.33\Omega$. Adding the remaining three resistances in series results in: $R_{\text{series}} = 1\Omega + 1.33\Omega + 3\Omega = 5.33\Omega$. We are given the power dissipated across one of the two resistors connected in parallel, so we can determine both the voltage and current across them. We can then use these currents to find the remaining resistor's current and voltage, which can then be used to determine the overall voltage output by the battery

EVALUATE From the power dissipated by the $4.0\text{-}\Omega$ resistor we find the voltage across the parallel resistance: $P_{4\Omega} = V_{\text{parallel}}^2 / R_{4\Omega} \rightarrow V_{\text{parallel}} = \sqrt{P_{4\Omega} R_{4\Omega}} = 0.8\text{V}$. Applying Ohm's law for both resistors connected in parallel we find the currents: $I_{2\Omega} = V_{\text{parallel}} / R_{2\Omega} = 0.4\text{A}$ and $I_{4\Omega} = V_{\text{parallel}} / R_{4\Omega} = 0.2\text{A}$. The sum of these currents is equal to the current which passes through both the $1.0\text{-}\Omega$ and $3.0\text{-}\Omega$ resistors, meaning we can find the voltage drop across both resistors: $V_{1\Omega} = I_{1\Omega} R_{1\Omega} = 0.6\text{V}$ and $V_{3\Omega} = I_{3\Omega} R_{3\Omega} = 1.8\text{V}$. The voltage of the battery is found by adding up voltage drops across these resistors and the equivalent resistance from the two parallel resistors:

$$V = V_{1\Omega} + V_{\text{parallel}} + V_{3\Omega} = 3.2\text{V}$$

ASSESS Note how, in solving this problem, we used Ohm's law to find, alternately, voltage and then current in different resistances.

- 36. INTERPRET** This problem asks for the voltage across a resistor that's part of a more complex circuit. We are told the resistance of all components, including that of the battery connected.

DEVELOP Approaching this problem like the original example, we will follow the steps in Tactics 25.1. We begin by finding the equivalent resistance of the two resistors connected in parallel:

$$R_{\text{parallel}} = (33.0\Omega)(47.0\Omega)/(33.0\Omega + 47.0\Omega) = 19.4\Omega$$

Adding the remaining three resistances (which includes R_1 and the internal resistance of the battery) in series results in:

$$R_{\text{series}} = 12.5\Omega + 33.0\Omega + 19.4\Omega = 64.9\Omega$$

We can apply Ohm's law to find the current which flows through this circuit and determine the voltage drop across R_{parallel} .

EVALUATE Applying Ohm's law for the effective resistance contributed from all components we find the current which flows through the circuit is: $I = V/R_{\text{series}} = 92.4\text{mA}$. Since this is the current that flows through all components in series, we find that the voltage which is found across the parallel resistors is equal to:

$$V_{\text{parallel}} = V - V_{\text{battery}} - V_1 = 6.00\text{ V} - 1.16\text{ V} - 3.05\text{ V} = 1.79\text{ V}$$

Where we have subtracted the voltage drops across the battery's internal resistance and R_1 .

ASSESS Note how, in solving this problem, we used Ohm's law to find, alternately, voltage and then current in different resistances.

- 37. INTERPRET** This problem asks for the power dissipated by a resistor that's part of a more complex circuit. We are told the resistance of all components and are treating the battery as ideal.

DEVELOP Approaching this problem like the original example, we will follow the steps in Tactics 25.1. We begin by finding the equivalent resistance of the two resistors connected in parallel:

$$R_{\text{parallel}} = (180\Omega)(68\Omega)/(180\Omega + 68\Omega) = 49.4\Omega$$

Adding the remaining three resistances in series results in:

$$R_{\text{series}} = 220\Omega + 49.4\Omega = 269.4\Omega$$

We can apply Ohm's law to find the current which flows through this circuit and use it to find the voltage, and ultimately the power dissipated, across R_3 .

EVALUATE Applying Ohm's law for the effective resistance contributed from all components we find the current which flows through the circuit is: $I = V/R_{\text{series}} = 33.4\text{ mA}$. Since this is the current that flows through all components in series, we find that the voltage which is found across the parallel resistors is equal to:

$$V_{\text{parallel}} = V - V_1 = 9.0\text{ V} - 7.35\text{ V} = 1.65\text{ V}$$

Where we have subtracted the voltage drops across R_1 . Since this is the voltage found across R_3 , we find the power dissipated by R_3 is equal to: $P_3 = V_{\text{parallel}}^2/R_3 = 40.0\text{ mW}$.

ASSESS Note how, in solving this problem, we used Ohm's law to find, alternately, voltage and then current in different resistances.

- 38. INTERPRET** This is a problem about a charging capacitor, and we want to find the time to reach a given voltage.

DEVELOP Equation 25.6, $V_C = \mathcal{E}(1 - e^{-t/RC})$, gives the voltage across a charging capacitor, so our plan is to solve this equation for the time t .

EVALUATE First we solve for the exponential term that contains the time: $e^{-t/RC} = 1 - \frac{V_C}{\mathcal{E}}$. Then we take the

natural logarithm of both sides: $-\frac{t}{RC} = \ln\left(1 - \frac{V_C}{\mathcal{E}}\right)$. Solving for t and plugging in the given numerical values gives:

$$t = -RC \ln\left(1 - \frac{V_C}{\mathcal{E}}\right) = 8.4\text{ s}$$

ASSESS The high capacitance of this camera's circuit will require a longer charging time than the one discussed in the original example.

- 39. INTERPRET** This is a problem about a charging capacitor, and we want to find the amount of charging resistance that will reduce the wait time of the camera flash from the preceding problem.

DEVELOP Equation 25.6, $V_C = \mathcal{E}(1 - e^{-t/RC})$, gives the voltage across a charging capacitor, so our plan is to solve this equation for the resistance R .

EVALUATE First we solve for the exponential term that contains the resistance: $e^{-t/RC} = 1 - \frac{V_C}{\mathcal{E}}$. Then we take the

natural logarithm of both sides: $-\frac{t}{RC} = \ln\left(1 - \frac{V_C}{\mathcal{E}}\right)$. Solving for R and plugging in the given numerical values gives:

$$R = \frac{-t}{C \ln\left(1 - \frac{V_C}{\mathcal{E}}\right)} = 1.5\text{ k}\Omega$$

ASSESS The high capacitance of this camera's circuit will require a larger voltage supplied and less charging resistance to decrease the time between flashes.

- 40. INTERPRET** This is a problem about a discharging capacitor, and we want to find the time to reach a given voltage.

DEVELOP Equation 25.8, $V = V_0 e^{-t/RC}$, gives the voltage across a discharging capacitor, so our plan is to solve this equation for the time t .

EVALUATE (a) First we solve for the exponential term that contains the time and then we take the natural logarithm of both sides: $-\frac{t}{RC} = \ln\left(\frac{V}{V_0}\right)$. Solving for t and plugging in the given numerical values gives:

$$t = -RC \ln(0.1) = 14 \text{ ms}$$

where we have solved for the time when the voltage reaches 10% of the given 2.5 kV for V_0 .

(b) To find the energy delivered during this time we calculate the initial energy stored in the fully charged capacitor and subtract from it the energy left over after it has depleted 90% of its voltage.

$$\Delta U = \frac{1}{2} C (V_0^2 - (0.1V_0)^2) = \frac{1}{2} C (0.99)V_0^2 = 464 \text{ J}$$

ASSESS Although 90% of the voltage is used, 99% of the available energy is delivered upon discharging.

- 41. INTERPRET** This is a problem about a discharging capacitor like the one described in the preceding problem, and we want to find an expression for the capacitance which will lead a to certain fraction of the voltage to discharge in a given time.

DEVELOP Equation 25.8, $V = V_0 e^{-t/RC}$, gives the voltage across a discharging capacitor. We can relate this expression to the fraction f of energy stored in the capacitor which is discharged by performing the same calculation as in part (b) of the preceding problem.

$$\Delta U = \frac{1}{2} C (1 - \phi^2) V_0^2 = f U_i$$

Here we have calculated the amount of energy discharged by subtracting the amount of energy left over after a time Δt , where the remaining voltage at time t is equal to $V(t) = \phi V_0$, meaning: $\phi = \sqrt{1 - f}$. Using this, we can express the voltage after a given time Δt and solve for the capacitance which would result in the desired fractional energy discharge.

EVALUATE Solving for the exponential term in Equation 25.8 and plug in the voltage found after a time Δt we find:

$$e^{-\Delta t/RC} = \frac{V}{V_0} = \phi = \sqrt{1 - f}$$

$$C = \frac{-2\Delta t}{R \ln(1 - f)}$$

ASSESS We can check the validity of this expression by plugging in the 99% of energy discharged from the preceding problem to recover the given capacitance of the defibrillator.

PROBLEMS

- 42. INTERPRET** This problem involves a multiloop circuit for which we are to find the resistance between the different points given.

DEVELOP The resistance between A and B is equivalent to two resistors of value R in series with the parallel combination of resistors of values R and $2R$. Thus, the equivalent resistance may be found by combining Equations 25.1 and 25.3b. R_{AC} is equivalent to just one resistor of value R in series with the parallel combination of R and $2R$ (since the resistor at point B carries no current, that is, its branch is an open circuit).

EVALUATE (a) $R_{AB} = R + R + R(2R)/(R + 2R) = 8R/3$. (b) $R_{AC} = R + R(2R)/(3R) = 5R/3$.

ASSESS $R_{AB} > R_{AC}$ because the stem B carries no current.

- 43. INTERPRET** This problem asks for the current in a resistor that is part of a more complex multiloop circuit. We will find the voltage drop over this resistor, which is part of a parallel combination of resistors, to find the current passing through it.

DEVELOP The circuit in Fig. 25.28, with a battery connected across points A and B , is similar to the circuit analyzed in Example 25.3. In this case, we have one $2.0\text{-}\Omega$ resistor in parallel with two $2.0\text{-}\Omega$ resistors in series. Thus, combining Equations 25.1 and 25.3b, we find

$$\frac{1}{R_{\parallel}} = \frac{1}{2.0\text{ }\Omega} + \frac{1}{2.0\text{ }\Omega + 2.0\text{ }\Omega} = \frac{3}{4\text{ }\Omega} \rightarrow R_{\parallel} = \frac{4}{3}\text{ }\Omega$$

and the total resistance is R_{\parallel} in series with two $2.0\text{-}\Omega$ resistors: $R_{\text{tot}} = 2.0\text{ }\Omega + 2.0\text{ }\Omega + \frac{4}{3}\text{ }\Omega = \frac{16}{3}\text{ }\Omega$. The total current through the battery is

$$I_{\text{tot}} = \frac{\mathcal{E}}{R_{\text{tot}}} = \frac{6.0\text{ V}}{16/3\text{ }\Omega} = 1.125\text{ A}$$

EVALUATE Using the macroscopic version of Ohm's law, the voltage across the parallel combination is

$$V_{\parallel} = I_{\text{tot}} R_{\parallel} = (1.125\text{ A})\left(\frac{4}{3}\text{ }\Omega\right) = 1.5\text{ V}$$

which is the voltage across the vertical $R_v = 2.0\text{-}\Omega$ resistor. Thus, the current through this resistor is then

$$I_v = \frac{V_{\parallel}}{R_v} = \frac{1.5\text{ V}}{2.0\text{ }\Omega} = 0.75\text{ A}$$

ASSESS We have a total of 1.125 A of current flowing around the circuit. At the vertex of the triangular loop, it is split into $I_v = 0.75\text{ A}$ and $I' = I_{\text{tot}} - I_v = 0.375\text{ A}$. The voltage drop across the vertical resistor ($V_{\parallel} = 1.5\text{ V}$) is the same as that going through point C and the two $2.0\text{-}\Omega$ resistors: $V' = (0.375\text{ A})(2.0\text{ }\Omega + 2.0\text{ }\Omega) = 1.5\text{ V}$. Thus, the result is consistent.

- 44. INTERPRET** We are to find (to three significant figures) the voltage across the terminals of a battery for three different internal resistances, and with a $2\text{-}\Omega$ resistor connected between the terminals.

DEVELOP The circuit diagram is like Fig. 25.9, and the voltage across the load (from Kirchhoff's voltage law) is $V_L = \mathcal{E} - IR_{\text{int}}$. Since $I = \mathcal{E} / (R_L + R_{\text{int}})$, we have $V_L = \mathcal{E} R_L / (R_L + R_{\text{int}})$ (as for a voltage divider).

EVALUATE With the given numerical values,

$$V_L = (1.5\text{ V})(2\text{ }\Omega) / (2\text{ }\Omega + R_{\text{int}}) = 1.49\text{ V}, 1.43\text{ V}, \text{ and } 1.0\text{ V}$$


for $R_{\text{int}} = 0.01\text{ }\Omega$, $0.1\text{ }\Omega$, and $1\text{ }\Omega$, respectively.

ASSESS Normally, because the data is given to a single significant figure, we should retain only a single significant figure in the result.

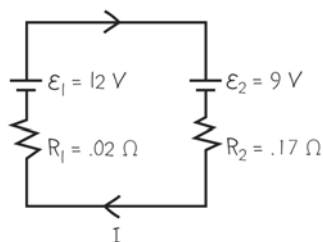- 45. INTERPRET** The circuit has two batteries connected in series. We will apply Kirchhoff's law to find the current that flows through the discharged battery.

DEVELOP Terminals of like polarity are connected with jumpers of negligible resistance, giving a circuit as shown below. Kirchhoff's voltage law gives

$$\mathcal{E}_1 - \mathcal{E}_2 - IR_1 - IR_2 = 0$$



EVALUATE Solving the equation above for I , we obtain

$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{12\text{ V} - 9\text{ V}}{0.02\text{ }\Omega + 0.17\text{ }\Omega} = 15.8\text{ A}$$

ASSESS When you try to jump-start a car, you connect positive to positive and negative to negative terminals. The current is quite significant, which is why you want to have the charged car running to prevent the battery from being drained.

- 46. INTERPRET** To check the safety of a battery, you must determine if a lethal dose of current could potentially flow through a person who is damp or sweaty.

DEVELOP The battery is not ideal. It has an internal resistance that will reduce the terminal voltage when current is flowing out of the battery. This internal resistance will be in series with the human body's resistance.

EVALUATE The total resistance will be the sum of the internal resistance and the human body's resistance. Therefore, the current that could potentially flow through a person with wet skin touching the battery terminals is

$$I = \frac{V}{R_{\text{int}} + R_{\text{human}}} = \frac{72 \text{ V}}{100 \Omega + 500 \Omega} = 120 \text{ mA}$$

Yes, this current could be fatal.


ASSESS You'll likely need to introduce a safety feature, such as a fuse, that can prevent such a high current from flowing out of the battery.

- 47. INTERPRET** We are given a purely resistive circuit consisting of three resistors in parallel combined in series with a single resistor and are to find the current through the battery and the current through the 6- Ω resistor.

DEVELOP Label the resistors as shown below. The current supplied by the battery may be found using Ohm's law, $V = IR_{\text{tot}}$, where R_{tot} is

$$R_{\text{tot}} = R_1 + R_{\parallel} = R_1 + \frac{R_2 R_3 R_4}{R_2 R_3 + R_3 R_4 + R_4 R_2} = 1 \Omega + \frac{(2 \Omega)(4 \Omega)(6 \Omega)}{(2 \Omega)(4 \Omega) + (4 \Omega)(6 \Omega) + (6 \Omega)(2 \Omega)} = 2.09 \Omega$$

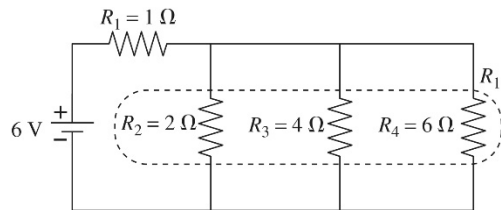where we have used Equation 25.1 and 25.3a to find the total resistance. The voltage drop across all three resistors in parallel is $V_{\parallel} = \mathcal{E} - IR_1 = IR_{\parallel}$, so the current through the 6- Ω resistor can be found using Ohm's law.



EVALUATE (a) The current through the battery is

$$I = \frac{V}{R_{\text{tot}}} = \frac{6 \text{ V}}{2.09 \Omega} = 2.9 \text{ A}$$

to a single significant figure.

(b) To a single significant figure, the current through the 6- Ω resistor is

$$V_{\parallel} = V - IR_1 = I_4 R_4$$

$$I_4 = \frac{V - IR_1}{R_4} = \frac{6 \text{ V} - (2.87 \text{ A})(1 \Omega)}{6 \Omega} = 0.52 \text{ A}$$

ASSESS The currents passing through R_2 and R_3 are

$$I_2 = \frac{V - IR_1}{R_2} = 1.57$$

$$I_3 = \frac{V - IR_1}{R_3} = 0.78$$

which, when summed with I_4 , give I , as expected. Notice that the smallest current runs through R_4 because it is the largest of the three parallel resistors.

- 48. INTERPRET** We are given access to three different types of resistors which all dissipate the same maximum power. We are to come up with two configurations that will result in an effective resistance of 6.0 Ω capable of safely connecting to a 3.0-V battery.

DEVELOP We have 1.5- Ω , 3.0- Ω , and 12- Ω resistors available, and we can choose to assemble these in any combination of series and parallel configurations. However, neither of the configurations can have any resistors exceed a power dissipation of $\frac{1}{2}$ W. Right away we can see that neither the 1.5- Ω or 3.0- Ω resistors can be safely connected in parallel with the battery while the 12- Ω resistors can. For series configurations, the order and total number of resistors will determine the amount dissipated in each component. Thus, we can first determine different configuration that will result in an effective resistance of 6.0 Ω , and then assess whether each resistor will dissipate less than or equal to $\frac{1}{2}$ W when connected across the battery.

EVALUATE The first possible configuration has four 1.5- Ω resistors in series summing to 6.0 Ω , where each resistor has $\frac{1}{2}$ A flowing through it, and experiences a voltage drop of $\frac{3}{4}$ V. This means that the power dissipated is equal to $P = IV = 3/8$ W, making it a safe configuration. A second possible configuration uses four of the 12- Ω resistors in parallel to obtain an effective resistance of $R_{||} = 3.0\Omega$, which is then placed in series with an identical set to obtain a final resistance of 6.0 Ω

$$R_{\text{tot}} = R_{||1} + R_{||2} = \left(\frac{4}{12\Omega} \right)^{-1} + \left(\frac{4}{12\Omega} \right)^{-1} = 6.0\Omega$$

In this configuration, the current flowing through both $R_{||1}$ and $R_{||2}$ is equal to $\frac{1}{2}$ A, meaning each resistor has $1/8$ A flowing through it. Since the voltage drop across both $R_{||1}$ and $R_{||2}$ is $3/2$ V, the power dissipated in each resistor is $P = IV = 3/16$ W, again making it a safe configuration.

ASSESS Is it possible to come up with a third different configuration which utilizes at least one of each type? Why or why not?

49. **INTERPRET** This problem asks for the power dissipated in a resistor that is part of a multiloop circuit.

DEVELOP The three resistors in parallel have an effective resistance of

$$\frac{1}{R_{||}} = \frac{1}{2\Omega} + \frac{1}{4\Omega} + \frac{1}{6\Omega} = \frac{11}{12\Omega} \Rightarrow R_{||} = \frac{12}{11}\Omega$$

The equivalent resistance of the circuit is $R_{\text{tot}} = R_1 + R_{||} = 1\Omega + \frac{12}{11}\Omega = \frac{23}{11}\Omega$. Equation 25.2 gives the voltage across them as

$$V_{||} = \frac{\varepsilon R_{||}}{R_{\text{tot}}} = \frac{(6\text{ V})(12/11\Omega)}{23/11\Omega} = \frac{72}{23}\text{ V}$$

EVALUATE Using Equation 24.8b, the power dissipated in the 2- Ω resistor is

$$P_2 = \frac{V_{||}^2}{R_2} = \frac{(72/23)^2}{2\Omega} = 4.9\text{ W}$$

ASSESS With ε held fixed at 6 V, we see that the power dissipated is inversely proportional to the resistance.


50. **INTERPRET** We are to find the ammeter reading when the ammeter is connected between the points of the multiloop circuit shown in the figure below.

DEVELOP Make a circuit diagram and label the currents and nodes as shown below. If the ammeter has zero resistance, the potential difference across it is zero, or nodes C and D are at equal potentials. If I is the current through the battery, $\frac{1}{2}I$ must go through each of the 2- Ω resistors connected at node A (Kirchhoff's current law), because the potential drop across them is the same. At node B , the 2- Ω resistor accepts twice the current of the 4- Ω resistor, or $\frac{2}{3}I$ and $\frac{1}{3}I$, respectively (the total current coming out of node B must be I , by Kirchhoff's current law). We thus know the currents I_{AC} and I_{CD} . By Kirchhoff's current law, the current going through the ammeter must be the difference of I_{AC} and I_{CD} , or

$$\begin{aligned} I_{\text{ammeter}} + I_{AC} - I_{CD} &= 0 \\ I_{\text{ammeter}} &= -\frac{I}{2} + \frac{2I}{3} = \frac{I}{6} \end{aligned}$$

To find the value of I , note that the upper pair of resistors are effectively in parallel because $V_C = V_D$, as is the lower pair. The effective resistance between A and B is therefore
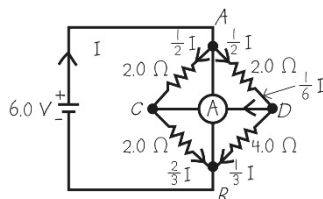
$$R_{\text{eff}} = \frac{(2\ \Omega)(2\ \Omega)}{2\ \Omega + 2\ \Omega} + \frac{(2\ \Omega)(4\ \Omega)}{2\ \Omega + 4\ \Omega} = 1\ \Omega + \frac{4}{3}\ \Omega = \frac{7}{3}\ \Omega$$



EVALUATE Using Ohm's law, we find that the ammeter reads

$$V = IR_{\text{eff}} = 6I_{\text{ammeter}}R_{\text{eff}}$$

$$I_{\text{ammeter}} = \frac{V}{6R_{\text{eff}}} = \frac{6\ \text{V}}{6(7\ \Omega/3)} = \frac{3}{7}\ \text{A}$$

ASSESS To a single significant figure, this is 0.43 A.

- 51. INTERPRET** We are to find the currents through each of the three resistors in the given circuit. We will use the circuit diagram given in Example 25.4.

DEVELOP The general solution of the two loop equations and the one node equation given in Example 25.4 can be found using determinants (or I_1 and I_2 can be found in terms of I_3 , as in Example 25.4). The equations and the solution are:

$$\begin{aligned} I_1 R_1 + 0 + I_3 R_3 &= \varepsilon_1 & (\text{loop 1}) \\ 0 - I_2 R_2 + I_3 R_3 &= \varepsilon_2 & (\text{loop 2}) \\ I_1 - I_2 - I_3 &= 0 & (\text{node A}) \end{aligned}$$

$$\Delta \equiv \begin{vmatrix} R_1 & 0 & R_3 \\ 0 & -R_2 & R_3 \\ 1 & -1 & -1 \end{vmatrix} = R_1 R_2 + R_2 R_3 + R_3 R_1 = (2\ \Omega)(4\ \Omega) + (2\ \Omega)(1\ \Omega) + (1\ \Omega)(4\ \Omega) = 14\ \Omega^2$$

$$I_1 = \frac{1}{\Delta} \begin{vmatrix} \varepsilon_1 & 0 & R_3 \\ \varepsilon_2 & -R_2 & R_3 \\ 0 & -1 & -1 \end{vmatrix} = \frac{\varepsilon_1(R_2 + R_3) - \varepsilon_2 R_3}{\Delta}$$

$$I_2 = \frac{1}{\Delta} \begin{vmatrix} R_1 & \varepsilon_1 & R_3 \\ 0 & \varepsilon_2 & R_3 \\ 1 & 0 & -1 \end{vmatrix} = \frac{\varepsilon_1 R_3 - \varepsilon_2(R_1 + R_3)}{\Delta}$$

$$I_3 = \frac{1}{\Delta} \begin{vmatrix} R_1 & 0 & \varepsilon_1 \\ 0 & -R_2 & \varepsilon_2 \\ 1 & -1 & 0 \end{vmatrix} = \frac{\varepsilon_2 R_1 + \varepsilon_1 R_2}{\Delta}$$

EVALUATE Using $\varepsilon_1 = 6\ \text{V}$ and $\varepsilon_2 = -9\ \text{V}$, we find

$$I_1 = \frac{(6\ \text{V})(4\ \Omega + 1\ \Omega)}{14\ \Omega^2} = 2.8\ \text{A}$$

$$I_2 = \frac{(6\ \text{V})(1\ \Omega) - (-9\ \text{V})(2\ \Omega + 1\ \Omega)}{14\ \Omega^2} = 2.4\ \text{A}$$

$$I_3 = \frac{(-9\ \text{V})(2\ \Omega) + (6\ \text{V})(4\ \Omega)}{14\ \Omega^2} = 0.43\ \text{A}$$

ASSESS From the signs of the currents, we know that I_1 flows down and I_2 and I_3 flow up. This is expected because the polarity of ε_2 is reversed with respect to Example 25.4, so the positive terminal of ε_1 is 15 V above the negative terminal of ε_2 , and the central node (above R_3) is at 9 V with respect to the negative terminal of ε_2 .

- 52. INTERPRET** This problem asks us to reconsider the circuit discussed in Example 25.4 with a reversed battery. We are to determine an expression for the current running through a resistor and the voltage necessary in the reversed battery to make this current zero.

DEVELOP We can treat this problem similarly to Example 25.4, applying Kirchhoff's node law to each loop, and treating each quantity generally, to obtain the two equations:

$$\mathcal{E}_1 - I_1 R_1 - I_1 R_3 = 0$$

$$\mathcal{E}_2 - I_3 R_3 + I_2 R_2 = 0$$

And again recognizing that the currents satisfy the equation: $-I_1 + I_3 + I_2 = 0$. We will use these to obtain an expression for the current I_3 in terms of the voltage \mathcal{E}_2 .

EVALUATE (a) We begin by rewriting the first loop equation as: $\mathcal{E}_1 - (I_2 + I_3) R_1 - I_1 R_3 = 0$, where solving for the current I_2 gives

$$I_2 = \frac{1}{R_1} (\mathcal{E}_1 - (R_1 + R_3) I_3)$$

which we then substitute into the second loop equation and simplify to:

$$\mathcal{E}_2 - I_3 R_3 + \left[\frac{1}{R_1} (\mathcal{E}_1 - (R_1 + R_3) I_3) \right] R_2 = 0$$

$$\mathcal{E}_2 + \frac{R_2}{R_1} \mathcal{E}_1 - I_3 \left[R_3 + \frac{R_2}{R_1} (R_1 + R_3) \right] = 0$$

$$I_3 = \frac{\left(\mathcal{E}_2 + \frac{R_2}{R_1} \mathcal{E}_1 \right)}{\left[R_3 + \frac{R_2}{R_1} (R_1 + R_3) \right]} = \frac{(12 + \mathcal{E}_2)}{7}$$

(b) For there to be no current flowing through R_3 , the current I_3 would need to equal 0, which is only possible when the voltage \mathcal{E}_2 is equal to -12 V.

ASSESS We can check that this expression for I_3 is valid for any value and sign of \mathcal{E}_2 by plugging in the $+9$ V used in Example 25.4 to recover the 3 A current found in the original problem.

- 53. INTERPRET** In this problem, we are to find the voltage across a given resistor as measured using a voltmeter, with the given internal resistances. Because the voltmeter is connected in parallel with the $30\text{-k}\Omega$ resistor, the voltmeter's resistance adds in parallel to the resistor's resistance.

DEVELOP With a meter of resistance R_m connected as indicated in the figure below, the circuit reduces to two pairs of parallel resistors in series. The total resistance is the sum of these parallel resistances (Equations 25.1 and 25.3b):


$$R_{\text{tot}} = \frac{(30 \text{ k}\Omega) R_m}{30 \text{ k}\Omega + R_m} + \frac{40 \text{ k}\Omega}{2}$$

Using Ohm's law (Chapter 24), the voltage reading is

$$V_m = R_m I_m = \frac{R_m (30 \text{ k}\Omega) I_{\text{tot}}}{30 \text{ k}\Omega + R_m}$$

where $I_{\text{tot}} = (100 \text{ V}) / R_{\text{tot}}$ (the expression for V_m follows from Equation 25.2, with R_1 and R_2 as the above pairs, or from I_m as a fraction of I_{tot}).

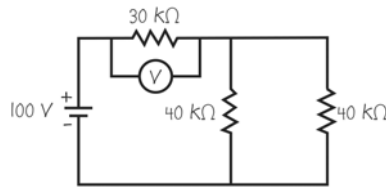EVALUATE For the three voltmeter resistances specified, $I_{\text{tot}} = 2.22 \text{ mA}$, 2.10 mA , and 2.00 mA , and $V_m = 55.5 \text{ V}$, 58 V , and 60 V , respectively.



ASSESS Of course, 60 V is the ideal voltmeter reading. This reading corresponds to an ideal voltmeter that has infinite resistance. Thus, to two significant figures, the 10-M Ω voltmeter is an ideal voltmeter.

- 54. INTERPRET** For this problem we are to find the voltage between points *A* and *B* assuming an ideal voltmeter is used and the current from *A* to *B* assuming we connect an ideal ammeter between the two points. Recall that an ideal voltmeter has infinite resistance and an ideal ammeter has zero resistance.

DEVELOP An ideal voltmeter has infinite resistance, so *AB* is still an open circuit (as shown on Fig. 25.34) when such a voltmeter is connected. Thus, the meter will read the voltage across the $R_2 = 36\text{-k}\Omega$ resistor. From Ohm's law, the current passing through the resistors is $I = V/(R_1 + R_2)$, so the voltage across R_2 will be

$$V_2 = V - IR_1 = V - \frac{VR_1}{R_1 + R_2} = V \left(\frac{R_2}{R_1 + R_2} \right)$$

Because an ideal ammeter has zero resistance, it will measure the current through the points *A* and *B* when they are short-circuited (i.e., no current flows through the 36-k Ω resistor). We can find this current by applying Ohm's law to R_1 .

EVALUATE (a) Inserting the values into the expression above, we find the voltage across R_2 , as measured by an ideal voltmeter, is

$$V_2 = V \left(\frac{R_2}{R_1 + R_2} \right) = (48 \text{ V}) \left(\frac{36 \text{ k}\Omega}{18 \text{ k}\Omega + 36 \text{ k}\Omega} \right) = 32 \text{ V}$$

(b) The current passing through the ideal ammeter connected to points *A* and *B* is

$$I = \frac{V}{R_1} = \frac{48 \text{ V}}{18 \text{ k}\Omega} = 2.7 \text{ mA}$$

ASSESS The current found in part (b) does not pass through R_2 , because R_2 seems like an infinite resistance compared to the zero-resistance ammeter. The current passing through R_2 when the ammeter is not connected is

$$I_2 = \frac{V_2}{R_2} = \frac{32 \text{ V}}{36 \text{ k}\Omega} = 0.89 \text{ mA}$$

which is less than the 2.7 mA because $R_2 > 0$.

- 55. INTERPRET** In this problem an ammeter is used to measure the current in a circuit. The ammeter is connected in series with the resistor. We consider both the ammeter and the battery as having some internal resistance.

DEVELOP When the considering an ideal battery and ammeter are the internal resistances are zero, and the resistor would have a value of simply given by $R = \mathcal{E}/I$. When considering the internal resistances of both, we must consider all three loads connected in series.

EVALUATE (a) Using the current the ammeter reads we find an unknown resistance of

$$R = \mathcal{E}/I = 18.25 \Omega$$

(b) If the internal resistance of both battery and ammeter are known, we can consider this to be the effective resistance of all three loads. Thus, subtracting the sum of the 116.0 m Ω of the ammeter and the 59.0 m Ω of the battery from the result of part (a) we find the actual resistance of the unknown resistor is equal to: 18.07 Ω .

(c) To obtain the percent error between the results we calculate

$$\frac{R' - R}{R} = \frac{18.25 - 18.07}{18.25} = 1\%$$

Meaning the result in part (a) was high by 1%.

ASSESS This is a small error, given that the measurement device should interfere as little as possible, and the battery should provide as much of its available voltage as possible.

- 56. INTERPRET** This problem involves an RC circuit, as shown in Fig. 25.18. We are to find the time required for the voltage across the capacitor to reach the given value, given the RC time constant. In addition, we are to find the capacitance, given the resistance of the circuit.

DEVELOP Equation 25.6 gives the voltage as a function of time for a charging capacitor. Given that the capacitor voltage at $t = 13 \text{ ms}$ is $V(t = 13 \text{ ms}) = \mathcal{E}(1 - 1/e)$, we can write

$$V(t = 13 \text{ ms}) = \mathcal{E}\left(1 - e^{-(13.0 \text{ ms})/RC}\right) = \mathcal{E}(1 - e^{-1})$$

which tells us that $(13.0 \text{ ms})/(RC) = 1$, or $RC = 13.0 \text{ ms}$. This allows us to find the time at which

$V(t) = \mathcal{E}(1 - e^{-3})$. To find the capacitance, we use the same result ($RC = 13.0 \text{ ms}$) and insert $R = 22 \text{ k}\Omega$.

EVALUATE (a) When $V(t) = \mathcal{E}(1 - e^{-3}) = \mathcal{E}(1 - e^{-t/RC})$, we have $t/RC = 3$, or $t = 3RC = 3(13.0 \text{ ms}) = 39 \text{ ms}$.

(b) For $R = 22 \text{ k}\Omega$, $C = (13.0 \text{ ms}) / (22 \text{ k}\Omega) = 0.59 \text{ }\mu\text{F}$.

ASSESS Thus, at 13.0 ms , the capacitor is $1 - e^{-1} = 63\%$ charged, whereas at 39 ms , the capacitor is $1 - e^{-3} = 95\%$ charged.

- 57. INTERPRET** You need to design a defibrillator that meets the desired discharge time. This is essentially an RC circuit, where the resistor is the human chest.

DEVELOP The defibrillator specs call for the capacitor to discharge to half its initial voltage in 10 ms . In terms of Equation 25.8, this implies: $e^{-t/RC} = \frac{1}{2}$. You can figure out the initial voltage using Equation 23.3: $U = \frac{1}{2}CV^2$.

EVALUATE Using $R = 33 \text{ }\Omega$ for the transthoracic resistance, the needed capacitance is to the nearest $10 \text{ }\mu\text{F}$:

$$C = \frac{-t}{R \ln\left(\frac{1}{2}\right)} = \frac{(10 \text{ ms})}{(33 \text{ }\Omega) \ln 2} = 440 \text{ }\mu\text{F}$$

Given that the stored energy in the capacitor is 250 J , the initial voltage must be to the nearest 100 V :

$$V_0 = \sqrt{\frac{2U}{C}} = \sqrt{\frac{2(250 \text{ J})}{(437 \text{ }\mu\text{F})}} = 1070 \text{ V}$$

ASSESS The initial current going through the chest is $I_0 = V_0/R = 32.4 \text{ A}$. Such a huge amount of current can sometimes cause burns (see Table 24.3). But the person will likely die if this “jolt” to the heart is not applied in time.

- 58. INTERPRET** This problem involves an RC circuit, for which we are to find the resistance and then find the capacitance required to maintain the voltage across the capacitor to within 1 V for $1/60 \text{ s}$.

DEVELOP The effective resistance can be found using Ohm’s law, given a voltage of $V = 35 \text{ V}$ and a current of $I = 1.2 \text{ A}$. To find the capacitance needed to maintain the voltage above 34 V , apply Equation 25.8, which describes the rate of discharge of a capacitor. To keep the voltage within the prescribed range for the discharging capacitor, the time constant must satisfy $V/V_0 = e^{-t/RC} \geq 34/35$, which allows us to solve for C using the value of R from part (a).

EVALUATE (a) The effective resistance of a circuit that draws 1.2 A from a constant 35-V supply is

$$R = \frac{V}{I} = \frac{35 \text{ V}}{1.2 \text{ A}} = 29 \text{ }\Omega$$

(b) Solving Equation 25.8 for the time constant, we find $RC \geq t/\ln(35/34)$. For $t = 1/60 \text{ s}$ and $R = 29.2 \text{ }\Omega$, the capacitance is $C \geq 20 \text{ mF}$.

ASSESS This is a rather large capacitance, which is necessary because it must discharge a large current of 1.2 A for $1/60 \text{ s}$.

- 59. INTERPRET** This problem involves energy dissipation in an RC circuit. Given the energy dissipated in the given time, we are to find the capacitance.

DEVELOP A capacitor discharging through a resistor is described by exponential decay, with time constant RC (Equation 25.8):

$$V(t) = V(0)e^{-t/RC}$$

The energy in the capacitor is given by Equation 23.3:

$$U_C(t) = \frac{1}{2}CV(t)^2 = \frac{1}{2}CV(0)^2 e^{-2t/RC} = U_C(0)e^{-2t/RC}$$

EVALUATE If 2 J is dissipated in time t , the energy stored in the capacitor drops from $U_C(0) = 5.0$ J to $U_C(t) = 3.0$ J (assuming there are no losses due to radiation, etc.). From the equation above, the capacitance is

$$C = \frac{2t}{R \ln[U_C(0)/U_C(t)]} = \frac{2(9.6 \text{ ms})}{(10 \text{ k}\Omega) \ln(5.0 \text{ J}/3.0 \text{ J})} = 3.8 \text{ }\mu\text{F}$$

ASSESS In this problem, the time constant is $RC = 38$ ms. Therefore, at 9.6 ms (about $0.253 RC$), the energy decreases by a factor $e^{-2(0.253)} \approx 0.6$, which is precisely what we found (i.e., from 5.0 V to $5.0 \times 0.6 = 3.0$ V).

60. INTERPRET The problem concerns what happens when a charged capacitor is connected to an uncharged capacitor. We'll worry about only the long-term behavior, that is, after the current has stopped flowing.

DEVELOP Initially, the charged capacitor has a charge of $Q_0 = C_2 V_0$, where the subscript "2" refers to the $2\text{-}\mu\text{F}$ capacitor. When the switch is closed, charge will flow from the charged capacitor to the uncharged capacitor until the voltage across both is equal. Since the final charge on each capacitor must sum up to the initial charge: $Q_1 + Q_2 = Q_0$, the final voltage must be

$$C_1 V_f + C_2 V_f = C_2 V_0 \rightarrow V_f = \frac{2 \text{ }\mu\text{F}}{1 \text{ }\mu\text{F} + 2 \text{ }\mu\text{F}} V_0 = \frac{2}{3} V_0$$

To find the total energy dissipated in the resistor, we find the difference between the stored energy in the initial and final states.

$$\Delta U = \left(\frac{1}{2} C_2 V_0^2 \right) - \left(\frac{1}{2} C_1 V_f^2 + \frac{1}{2} C_2 V_f^2 \right) = \left(\frac{5}{18} C_2 - \frac{4}{18} C_1 \right) V_0^2$$

EVALUATE Plugging in the values for the capacitors and the initial voltage, the energy dissipated in the resistor is

$$E = \Delta U = \left[\frac{5}{18} (2 \text{ }\mu\text{F}) - \frac{4}{18} (1 \text{ }\mu\text{F}) \right] (290 \text{ V})^2 = 28 \text{ mJ}$$

ASSESS Notice that the answer does not depend on the resistor's resistance. We might convince ourselves that this makes sense by looking at a simpler situation: a single capacitor discharging through a resistor, as in Fig. 25.22. The total energy dissipated by the resistor is the time integral of the power:

$$E = \int_0^\infty P dt = \int_0^\infty I^2 R dt = \frac{V_0^2}{R} \int_0^\infty e^{-2t/RC} dt = \frac{1}{2} C V_0^2$$

This is the initial energy stored in the capacitor. We can imagine, therefore, that the two-capacitor situation is similar: the resistor dissipates the energy lost by the charged capacitor. The amount of resistance in the resistor will affect only how fast the energy is dissipated.

61. INTERPRET This problem is about the long-term and short-term behavior of an RC circuit. For each extreme, we are to find the voltage and current in both resistors of the RC circuit of Example 25.6.

DEVELOP In addition to the explanation in Example 25.7, we note that when the switch is closed, Kirchhoff's voltage law applied to the loop containing both resistors yields $\mathcal{E} = I_1 R_1 + I_2 R_2$, and Kirchhoff's law applied to the loop containing just R_2 and C is $V_C = I_2 R_2$.

EVALUATE (a) If the switch is closed at $t = 0$, the circuit behaves as if it were the circuit of Fig. 25.23b, and Example 25.6 explains that $V_C(0) = 0$, $I(0) = 0$; so

$$I_1(0) = \frac{\mathcal{E}}{R_1} = \frac{150 \text{ V}}{4.0 \text{ k}\Omega} = 37.5 \text{ mA}$$

(b) As $t \rightarrow \infty$, the circuit behaves like the circuit of Fig. 25.23c, and Example 25.7 shows that

$$I_1(\infty) = I_2(\infty) = \frac{\mathcal{E}}{R_1 + R_2} = \frac{150 \text{ V}}{10 \text{ k}\Omega} = 15 \text{ mA}$$

and $V_C(\infty) = I_2(\infty)R_2 = (15 \text{ mA})(6.0 \text{ k}\Omega) = 90 \text{ V}$.

(c) Under the conditions stated, the fully charged capacitor ($V_C = 90 \text{ V}$) simply discharges through R_2 . (R_1 is in an open-circuit branch, so $I_1 = 0$ for the entire discharging process.) The initial discharging current is

$$I_2 = \frac{V_C}{R_2} = \frac{90 \text{ V}}{6.0 \text{ k}\Omega} = 15 \text{ mA}$$

(d) After a very long time, I_2 and V_C decay exponentially to zero.

ASSESS We deduced the short-term and long-term behavior of the RC circuit without having to solve a complicated differential equation. A long time after the circuit has been closed, the capacitor becomes fully charged and no more current can cross it, so it behaves as an open circuit. When the circuit switch is reopened, the capacitor starts to discharge and eventually loses all its stored energy. It is now capable of storing charge again and behaves like a short circuit for times much less than its RC time constant.

62. INTERPRET We're asked to find the short-term and long-term behavior of a complicated RC circuit.

DEVELOP Right after the switch is closed, the two capacitors will act like short-circuits, that is, like wires with zero resistance. Current will flow through them in preference to any parallel resistors. Much later, the capacitors will be nearly fully charged, in which case they will act like an open circuit. No more current will flow through them.

EVALUATE (a) When the switch is closed, the capacitor C_1 in Fig. 25.36 will offer an essentially zero-resistance pathway for current from the emf to flow. Therefore, no current will flow through R_2 , or R_3 for that matter. If we label the currents by the resistor they go through: $I_1 = \mathcal{E} / R_1$, $I_2 = I_3 = 0$.

(b) Long after the switch is closed, both capacitors C_1 and C_2 will be charged, so no more current will flow into these two branches of the circuit. All of the current from the emf will now flow through R_2 , which means $I_1 = I_2 = \mathcal{E} / 2R$, and $I_3 = 0$.

ASSESS One can easily guess that I_1 and I_2 respectively decrease and increase monotonically from their initial to their final values, and that I_3 first increases from, and then decreases to zero.

63. INTERPRET We are asked to find the voltage and internal resistance of a battery using the measured voltage values of two voltmeters with different internal resistances.


DEVELOP The internal resistance R_i of the battery and the resistance R_m of the voltmeter are in series with the battery's internal emf (see circuit below), so the current is $I = \mathcal{E} / (R_i + R_m)$. The potential drop across the meter (its reading) is

$$V_m = IR_m = \frac{\mathcal{E}R_m}{R_i + R_m}$$

From the given data, we can write

$$4.36 \text{ V} = \frac{\mathcal{E}(10.00 \text{ k}\Omega)}{R_i + 10.00 \text{ k}\Omega} \text{ and } 4.41 \text{ V} = \frac{\mathcal{E}(14.00 \text{ k}\Omega)}{R_i + 14.00 \text{ k}\Omega}$$
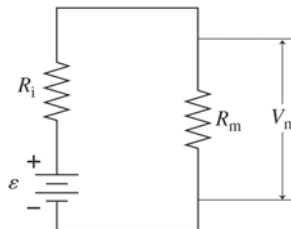
$$\text{or } R_i + 10.00 \text{ k}\Omega = \mathcal{E}(10.00 \text{ k}\Omega) / (4.36 \text{ V}) \text{ and } R_i + 14.00 \text{ k}\Omega = \mathcal{E}(14.00 \text{ k}\Omega) / (4.41 \text{ V})$$



EVALUATE Solving the simultaneous equations for \mathcal{E} and R_i gives

$$\mathcal{E} = 4.54 \text{ V and } R_i = 413 \Omega$$

ASSESS When we let $R_i \rightarrow 0$, its reading approaches the battery's internal emf \mathcal{E} .

64. INTERPRET We are asked to find the voltage and internal resistance of a battery using the measured voltage values of two ammeters with different internal resistances.

DEVELOP The internal resistance R_i of the battery and the resistance R_m of the ammeter are in series with the battery's internal emf, so the current is $I = \mathcal{E}/(R_i + R_m)$. From the given data, we can write

$$\mathcal{E} = (9.78 \text{ A})(1.42 \Omega + R_i) \quad \text{and} \quad \mathcal{E} = (7.46 \text{ A})(2.11 \Omega + R_i)$$

Equating the two expressions allows us to solve for R_i .

EVALUATE (b) Solving the equation $(9.78 \text{ A})(1.42 \Omega + R_i) = (7.46 \text{ A})(2.11 \Omega + R_i)$ gives

$$R_i = \frac{(7.46 \text{ A})(2.11 \Omega) - (9.78 \text{ A})(1.42 \Omega)}{9.78 \text{ A} - 7.46 \text{ A}} = 0.799 \Omega$$

(a) The battery's internal emf is

$$\mathcal{E} = (9.78 \text{ A})(1.42 \Omega + 0.799 \Omega) = 21.7 \text{ V}$$

ASSESS An ideal ammeter has zero resistance.

- 65. INTERPRET** This problem asks for the current through a resistor that is part of a more complex, multiloop circuit. The solution requires analyzing a circuit using Kirchhoff's laws.

DEVELOP Applying Kirchhoff's law to the right loop and the big loop gives

$$\begin{aligned} I_1 &= I_2 + I_3 \\ \mathcal{E}_1 - I_1 R_1 - I_3 R_3 + \mathcal{E}_3 &= 0 \quad (\text{big loop}) \\ \mathcal{E}_2 - I_3 R_3 + \mathcal{E}_3 + I_2 R_2 &= 0 \quad (\text{right loop}) \end{aligned}$$

The three equations allow us to solve for the three currents.

EVALUATE Solving for I_2 , we find

$$I_2 = \frac{(\mathcal{E}_1 - \mathcal{E}_2)R_3 - (\mathcal{E}_2 + \mathcal{E}_3)R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{(12.0 \text{ V} - 6.00 \text{ V})(4.00 \Omega) - (6.00 \text{ V} + 3.00 \text{ V})(1.00 \Omega)}{(1.00 \Omega)(2.00 \Omega) + (1.00 \Omega)(4.00 \Omega) + (2.00 \Omega)(4.00 \Omega)} = \frac{15}{14} \text{ A} = 1.07 \text{ A}$$

The direction is from left to right.

ASSESS The currents through R_1 and R_2 are

$$\begin{aligned} I_1 &= \frac{(\mathcal{E}_1 + \mathcal{E}_3)R_2 + (\mathcal{E}_1 - \mathcal{E}_2)R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{27}{7} \text{ A} = 3.86 \text{ A} \\ I_3 &= \frac{(\mathcal{E}_1 + \mathcal{E}_3)R_2 + (\mathcal{E}_2 + \mathcal{E}_3)R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{39}{14} \text{ A} = 2.79 \text{ A} \end{aligned}$$

One can verify that $I_1 = I_2 + I_3$.

- 66. INTERPRET** This problem involves a multiloop circuit. We find the condition such that no current goes through \mathcal{E}_2 . The solution requires analyzing a circuit using Kirchhoff's laws.

DEVELOP Applying Kirchhoff's law to the right loop and the big loop gives

$$\begin{aligned} I_1 &= I_2 + I_3 \\ \mathcal{E}_1 - I_1 R_1 - I_3 R_3 + \mathcal{E}_3 &= 0 \quad (\text{big loop}) \\ \mathcal{E}_2 - I_3 R_3 + \mathcal{E}_3 + I_2 R_2 &= 0 \quad (\text{right loop}) \end{aligned}$$

The three equations allow us to solve for the three currents. Solving for I_2 , we find

$$I_2 = \frac{(\mathcal{E}_1 - \mathcal{E}_2)R_3 - (\mathcal{E}_2 + \mathcal{E}_3)R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

The condition that no current goes through \mathcal{E}_2 implies $I_2 = 0$.

EVALUATE (a) Setting $I_2 = 0$ gives

$$(\mathcal{E}_1 - \mathcal{E}_2)R_3 - (\mathcal{E}_2 + \mathcal{E}_3)R_1 = 0$$

Solving for \mathcal{E}_2 , we obtain

$$\mathcal{E}_2 = \frac{\mathcal{E}_1 R_3 - \mathcal{E}_3 R_1}{R_1 + R_3} = \frac{(12.0 \text{ V})(4.00 \Omega) - (3.00 \text{ V})(1.00 \Omega)}{1.00 \Omega + 4.00 \Omega} = 9.00 \text{ V}$$

(b) Under these conditions, the currents in R_1 and R_3 are

$$I_1 = I_3 = \frac{(\mathcal{E}_1 + \mathcal{E}_3)R_2 + (\mathcal{E}_1 - \mathcal{E}_2)R_3}{R_1R_2 + R_1R_3 + R_2R_3} = \frac{(12.0 \text{ V} + 3.00 \text{ V})(2.00 \Omega) + (12.0 \text{ V} - 9.00 \text{ V})(4.00 \Omega)}{(1.00 \Omega)(2.00 \Omega) + (1.00 \Omega)(4.00 \Omega) + (2.00 \Omega)(4.00 \Omega)} = 3.00 \text{ A}$$

ASSESS One can also explore conditions that give $I_1 = 0$ or $I_3 = 0$. The required conditions would be:

$$I_1 = 0 \Rightarrow (\mathcal{E}_1 + \mathcal{E}_3)R_2 + (\mathcal{E}_1 - \mathcal{E}_2)R_3 = 0$$

$$I_3 = 0 \Rightarrow (\mathcal{E}_1 + \mathcal{E}_3)R_2 + (\mathcal{E}_2 + \mathcal{E}_3)R_1 = 0$$


- 67. INTERPRET** Using the data provided of the capacitor voltage as a function of time, we are to find the capacitance of the RC circuit.

DEVELOP From Equation 25.8, the voltage across the discharging capacitor is $V_C = \mathcal{E}e^{-t/RC}$. Thus, we see that the voltage V_C across the capacitor decreases exponentially to zero as $t \rightarrow \infty$. Thus, taking logarithm on both sides of the equation gives

$$\ln V_C = \ln \mathcal{E} - \frac{1}{RC}t$$

Plotting $\ln V_C$ versus t will then give a straight line with slope $-1/RC$.

EVALUATE The plot is shown below.

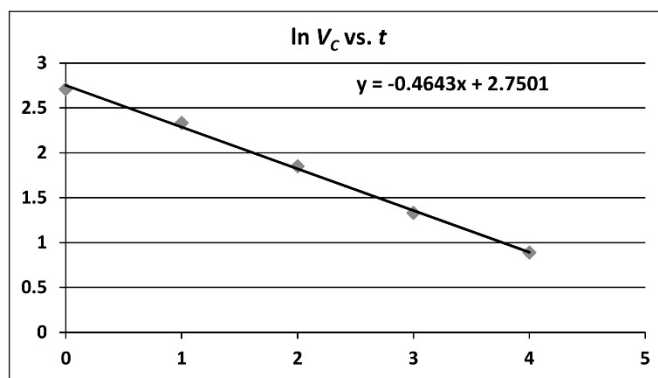

The slope of the straight-line fit is $-0.4643 = -1/RC$, from which we find the capacitance to be

$$C = \frac{1}{0.4643R} = \frac{1}{0.4643(1.0 \times 10^6)} = 2.15 \times 10^{-6} \text{ F} = 2.15 \mu\text{F}$$

ASSESS From the plot, we see that the y -intercept corresponds to $\ln \mathcal{E}$, which allows us to deduce the initial voltage across the capacitor:

$$\ln \mathcal{E} = 2.7501 \Rightarrow \mathcal{E} = 15.6 \text{ V}$$

- 68. INTERPRET** We are to find the resistance necessary in an RC circuit (see Fig. 25.18) to charge the given capacitor to 41% charge in 140 ms.

DEVELOP Apply Equation 25.6, which describes the voltage across a capacitor as a function of time.

EVALUATE Setting $V_C / \mathcal{E} = 41\%$ and solving for the RC time constant in Equation 25.6, we find

$$RC = \frac{t}{-\ln(1.00 - 0.41)} = \frac{140 \text{ ms}}{-\ln(0.59)} = 265 \text{ ms}$$

For a $20 \mu\text{F}$ capacitor, the resistance must be

$$R = \frac{265 \text{ ms}}{C} = \frac{265 \text{ ms}}{20 \mu\text{F}} = 13.25 \text{ k}\Omega$$

ASSESS Notice that a higher resistance would increase the time constant, so it would take longer to charge the capacitor, whereas a small resistance would have the reverse effect.

- 69. INTERPRET** The electric field at the node increases due to charge accumulation and eventually reaches the breakdown field strength. We are to find how long this process will take, given the rate at which charge accumulates on the sphere.

DEVELOP The charge on the node (whether positive or negative) accumulates at a rate of

$I = dq/dt = 1 \text{ A} = 1 \mu\text{C/s}$, so $|q(t)| = (1 \mu\text{A})t$ (where we assume that $q(0) = 0$). If the node is treated approximately as an isolated sphere, and if we assume that the charge distribution on the sphere becomes uniform at a rate much higher than the input current (so that we can treat it as a static distribution), then we can apply Gauss's law and the results of Example 21.1. Under these conditions, the electric field strength at the surface of the sphere is given as

$$E = \frac{k|q|}{r^2} = \frac{kIt}{r^2}$$

Electric breakdown occurs when $E = E_b = 3 \text{ MV/m}$.

EVALUATE The time when the breakdown happens is

$$t = \frac{E_b r^2}{kI} = \frac{(3 \text{ MV/m})(1.0 \text{ mm})^2}{(9 \times 10^9 \text{ m/F})(1 \mu\text{A})} = 0.3 \text{ ms}$$

to a single significant figure.

ASSESS This problem shows that Kirchhoff's node law must hold, or else there would be a charge buildup at the node that quickly leads to an electric breakdown.

- 70. INTERPRET** We want to find what load resistance connected to a battery will result in the greatest power output.

DEVELOP A real battery has an internal resistance, as shown in Fig. 25.8. When an external load is connected to the battery, the current that flows out will be $I = \mathcal{E} / (R_{\text{int}} + R_L)$. We want to find what R_L will give the maximum power: $P = I^2 R_L$.

EVALUATE The power will be a maximum when its derivative with respect to R_L is zero:

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left[\frac{\mathcal{E}^2 R_L}{(R_{\text{int}} + R_L)^2} \right] = \mathcal{E}^2 \left[\frac{1}{(R_{\text{int}} + R_L)^2} - \frac{2R_L}{(R_{\text{int}} + R_L)^3} \right] = 0$$

The equation is solved when $2R_L = R_{\text{int}} + R_L$, or $R_L = R_{\text{int}}$.

ASSESS The internal resistance of a battery is typically pretty low, so connecting a load with the same resistance would be essentially short-circuiting the battery. This could cause the battery to heat up and explode.

- 71. INTERPRET** You need to specify what loudspeaker resistance is needed to get the maximum power output from an amplifier.

DEVELOP The loudspeaker resistance will be in series with the amplifier's internal resistance. This is similar to the previous problem, where it was shown that the maximum power in the load (the loudspeaker, in this case) occurs when its resistance matches the internal resistance of the power supply.

EVALUATE From the above arguments, the optimum resistance for the loudspeaker is 7Ω . Since this is the same as the internal resistance of the amplifier, R_{int} , the power output will be:

$$P_{\text{max}} = \frac{\mathcal{E}^2 R_{\text{int}}}{(R_{\text{int}} + R_{\text{int}})^2} = \frac{\mathcal{E}^2}{4R_{\text{int}}}$$

If a loudspeaker with 3.5Ω of resistance is connected instead, the power is reduced by

$$P = \frac{\mathcal{E}^2 \left(\frac{1}{2} R_{\text{int}} \right)}{\left(R_{\text{int}} + \frac{1}{2} R_{\text{int}} \right)^2} = \frac{2\mathcal{E}^2}{9R_{\text{int}}} = \frac{8}{9} P_{\text{max}}$$

The maximum power is specified as 110 W , so a $3.5\text{-}\Omega$ loudspeaker will output 97.8 W .

ASSESS A loudspeaker with half the optimum resistance still produces almost 90% of the maximum power. This shows that it's not necessary to exactly match the load to the amplifier.

- 72. INTERPRET** This problem explores the energy stored in the capacitor of an RC circuit. We are asked to show that the capacitor stores only half the energy supplied by the battery.

DEVELOP The power supplied by the battery in charging an initially uncharged capacitor in an RC circuit is (Equation 24.7)

$$P = I\mathcal{E} = \frac{\mathcal{E}^2}{R} e^{-t/(RC)}$$

where the current is given by Equation 25.5, $I = (\mathcal{E}/R)e^{-t/(RC)}$. The total energy supplied by the battery is thus

$$U_{\text{battery}} = \int_0^{\infty} P dt = \frac{\mathcal{E}^2}{R} \int_0^{\infty} e^{-t/RC} dt = C\mathcal{E}^2 (e^0 - e^{-\infty}) = C\mathcal{E}^2$$

which we can compare with the energy stored in the capacitor (Equation 2.3.3), $U = CV^2/2$, where V is the final voltage across the capacitor.

EVALUATE The energy stored in the fully charged capacitor is

$$U_C(\infty) = \frac{1}{2} CV(t=\infty)^2 = \frac{1}{2} C\mathcal{E}^2 = \frac{1}{2} U_{\text{battery}}$$

Thus, we see that the energy stored in the capacitor is only half of that supplied by the battery.


ASSESS The other half of the energy supplied by the battery is dissipated in the resistor:

$$U_R = \int_0^{\infty} I^2 R dt = \frac{\mathcal{E}^2}{R} \int_0^{\infty} e^{-2t/RC} dt = \frac{1}{2} C\mathcal{E}^2$$

Notice that this result is independent of the value of the resistance and capacitance of the circuit.

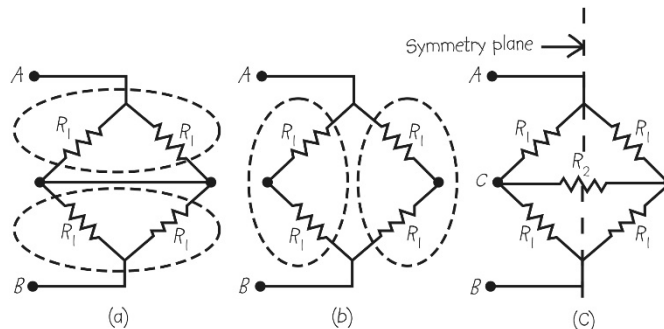73. INTERPRET We're asked to determine the equivalent resistance for several complex systems of resistors.

DEVELOP The circuit in (a) can be seen as two resistors in parallel followed in series by another pair of resistors in parallel. See the figure below. The circuit in (b) can be seen as two parallel branches, each with two resistors in series. The circuit in (c) is symmetric across a plane through the middle, so the same amount of current should flow through each side.



EVALUATE (a) Each pair of parallel resistors has an equivalent resistance of $R_{\parallel} = \frac{1}{2} R_1$. Added together in series, the total resistance is (Equation 25.1):

$$R_{\text{eq}} = R_{\parallel} + R_{\parallel} = R_1$$

(b) Each branch of resistors in series has an equivalent resistance of $R_s = 2R_1$. Added together in parallel, the total resistance is (Equation 25.3b):

$$R_{\text{eq}} = \frac{R_s \cdot R_s}{R_s + R_s} = R_1$$

(c) Due to the symmetry, the potential will be the same on both sides of R_2 , therefore no current will flow through this resistor. If there's no current through this branch, then the circuit is identical to the one in part (b), which means $R_{\text{eq}} = R_1$.

ASSESS Note that the reasoning in parts (a) and (b) is easily generalized to resistances of different values; the generalization in part (c) requires the equality of ratios of resistances that are mirror images in the plane of symmetry.

- 74. INTERPRET** This problem involves finding the voltage and internal resistance of a battery. We are given the current values when the battery is connected to two resistors of known resistance.

DEVELOP The circuit diagram is like Fig. 25.8, and Kirchhoff's voltage law gives

$$\mathcal{E} - IR_{\text{int}} - IR_L = 0$$

For the two different resistors given, this may be written as

$$\mathcal{E} - (26 \text{ mA})R_{\text{int}} = (26 \text{ mA})(50 \Omega) = 1.3 \text{ V}$$

$$\mathcal{E} - (43 \text{ mA})R_{\text{int}} = (43 \text{ mA})(21 \Omega) = 0.9 \text{ V}$$

EVALUATE (a) and (b) Solving for \mathcal{E} and R_{int} , we find

$$R_{\text{int}} = 23.5 \Omega$$

$$\mathcal{E} = 1.91 \text{ V}$$

ASSESS The terminal voltage of the battery is $V = \mathcal{E} - IR_{\text{int}} = 1.91 \text{ V} - I(23.5 \Omega)$, which is lower than \mathcal{E} . When the battery is connected to a resistor of resistance R , the current in the circuit is $I = \mathcal{E} / (R + R_{\text{int}})$.

- 75. INTERPRET** This problem explores the rate of increase in voltage across the capacitor of an RC circuit. We are to show that if the capacitor were to charge at its initial rate of charging (i.e., the rate at $t = 0$), then it would charge completely in a single time constant $\tau = RC$.

DEVELOP Kirchhoff's loop law for a battery charging a capacitor through a resistor is

$$\mathcal{E} - IR - V_C = 0$$

Differentiate this and use Equation 25.4 to obtain

$$\frac{dV_C(t)}{dt} = \frac{d[\mathcal{E} - I(t)R]}{dt} = -R \left[\frac{dI(t)}{dt} \right]$$

Using $I(t) = (\mathcal{E}/R)e^{-t/(RC)}$ for a charging capacitor (Equation 25.5), we find

$$\frac{dV_C(t)}{dt} = -R \frac{-I(t)}{RC} = \frac{I(t)}{C}$$

For an initially uncharged capacitor, $I(t=0) = \mathcal{E}/R \equiv I_0$, because an uncharged capacitor acts like a short-circuit. Thus, the initial rate of increase in voltage across the capacitor is

$$\frac{dV_C(t=0)}{dt} = \frac{\mathcal{E}}{RC} = \frac{\mathcal{E}}{\tau}$$

so we find how long it takes at this rate for the capacitor to be fully charged [i.e., to reach $V(t=\infty)$].

EVALUATE From Equation 25.6, we see that $V(t=\infty) = \mathcal{E}$, so charging at the above rate, the time t it would take to reach this voltage is

$$t \left[\frac{dV_C(t=0)}{dt} \right] = t \left(\frac{\mathcal{E}}{\tau} \right) = V(t=\infty) = \mathcal{E}$$

$$t \left(\frac{\mathcal{E}}{\tau} \right) = \mathcal{E} \Rightarrow t = \tau$$

ASSESS The real time it takes to reach full charge is longer than one time constant because the rate of change in the voltage is not constant.

- 76. INTERPRET** Our circuit consists of an array of resistors of infinite extent, and we're asked to find the equivalent resistance.

DEVELOP Since the circuit line is infinite, the addition or deletion of one more element leaves the equivalent resistance unchanged. This can be represented diagrammatically as



The right-hand picture represents R in series with the parallel combination R and R_{eq} . Thus,

$$R_{\text{eq}} = R + \frac{RR_{\text{eq}}}{R + R_{\text{eq}}}$$

EVALUATE Solving for R_{eq} , one finds $R_{\text{eq}}^2 - RR_{\text{eq}} - R^2 = 0$, or

$$R_{\text{eq}} = \left(1 + \sqrt{5}\right) \frac{R}{2} = 1.62R$$

Note that only the positive root is physically meaningful for a resistance.

ASSESS Let's see how this limiting value is reached. With only two resistors, the equivalent resistance is $R_1 = R + R = 2R$. Next, consider four resistors (the four on the left of Fig. 25.41). The equivalent resistance is


$$R_2 = R + \frac{1}{1/R + 1/2R} = R + \frac{2R}{3} = 1.67R$$

Continuing the same line of reasoning leads to the quadratic equation that we solved to obtain

$$R_{\text{eq}} = \left(1 + \sqrt{5}\right) R/2 = 1.62R.$$

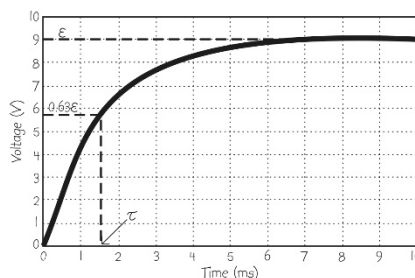- 77. INTERPRET** Using the plot provided of the capacitor voltage as a function of time, we are to find the battery voltage, time constant, and capacitance of the RC circuit.

DEVELOP From Equation 25.6, $V_C = \mathcal{E}(1 - e^{-t/(RC)})$, we see that the voltage V_C across the capacitor asymptotically approaches the battery voltage \mathcal{E} as $t \rightarrow \infty$. Thus, we can read the battery voltage off the graph by finding the asymptotic limit of the capacitor voltage (see the figure below). The time constant is the time it takes the capacitor voltage to reach $1 - e^{-1} = 63\%$ of its asymptotic value, as marked on the graph. From this estimate of the time constant τ , we can find the capacitance from using $\tau = RC$.



EVALUATE (a) From the asymptotic value of the capacitor voltage, we find that the battery voltage is $\mathcal{E} \sim 9$ V.

(b) In one time constant t , the capacitor reaches $\mathcal{E}(1 - e^{-1}) \approx (9 \text{ V})(0.63) = 5.7$ V. From the graph, this occurs at approximately $\tau \sim 1.5$ ms.

(c) The time constant is RC , so $C = \tau/R \approx (1.5 \text{ ms})/4700 \, \Omega \approx 0.3 \, \mu\text{F}$.

ASSESS From the graph, we can also see that the rate of increase of the capacitor voltage within one time constant is approximately linear, with a rate of

$$\frac{dV_C}{dt} \approx \frac{\mathcal{E}(1 - e^{-1})}{\tau} \approx \frac{2\mathcal{E}}{3\tau}$$

- 78. INTERPRET** This problem asks for the current through an emf source that is part of a more complex, multiloop circuit. The solution requires analyzing a circuit with series and parallel components.

DEVELOP Consider the circuit diagram below, with the currents assumed as indicated. Applying Kirchhoff's law to the right loop and the big loop gives

$$I_a + I_b + I_c = 0 \quad (\text{top node})$$


$$I_a(2R) - I_b(2R) = \mathcal{E}_1 - \mathcal{E}_3 \quad (\text{big loop})$$

$$I_b(2R) - I_c R = \mathcal{E}_3 - \mathcal{E}_2 \quad (\text{right loop})$$

Solve for I_a and I_c from the loop equations and substitute into the node equation:

$$\frac{(\varepsilon_1 - \varepsilon_3) + 2RI_b}{2R} + I_b + \frac{2RI_b - (\varepsilon_3 - \varepsilon_2)}{R} = 0$$

The current in ε_3 is I_b .

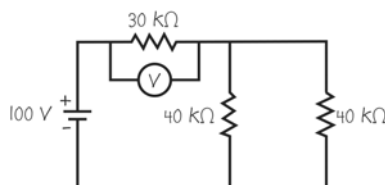

EVALUATE Solving for I_b , we find

$$I_b = \frac{(3\varepsilon_3 - 2\varepsilon_2 - \varepsilon)}{8R} = \frac{(60 \text{ mV} - 90 \text{ mV} - 75 \text{ mV})}{8(1.0 \text{ M}\Omega)} = -13.1 \text{ nA}$$

The negative sign means that the direction of I_b is opposite to that shown in the diagram.

ASSESS The negative sign in I_b can be easily understood by noting that ε_3 is smaller than ε_1 and ε_2 .

- 79. INTERPRET** This problem is an extension of the previous problem. The emf ε_3 changes now so that it supplies the indicated current. The rest of the circuit elements remain the same and we are to find the new value of ε_3 .

DEVELOP The relation between I_b and the circuit emf's and resistances, given in the solution to Problem 78, can be solved for ε_3 in Fig. 25.40, resulting in $\varepsilon_3 = \frac{1}{3}(8RI_b + 2\varepsilon_2 + \varepsilon_1)$.

EVALUATE For $I_b = 40 \text{ nA}$ and with the rest of the circuit elements remaining the same,

$$\varepsilon_3 = \frac{1}{3}(8 \times 1.5 \text{ M}\Omega \times 40 \text{ nA} + 90 \text{ mV} + 75 \text{ mV}) = 220 \text{ mV}$$

ASSESS Thus, ε_3 changes by an order of magnitude from 20 mV (in Problem 25.72) to 220 mV here.

- 80. INTERPRET** We will use Kirchhoff's laws to write a system of equations for the circuit shown in Fig. 25.27, and from the resulting equations we are to determine the possible values for the resistance R_3 .

DEVELOP We are told the values of resistors R_1 and R_2 , as well as the voltage across points A and B , and the power dissipated by resistor R_3 . This means we can determine a general expression for the current across the effective resistance R_{123} .

$$R_{123} = R_1 + R_{23} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

by noting that R_1 is in series with the effective resistance R_{23} resulting from the parallel arrangement of resistors R_2 and R_3 . We will use it to find the current I_3 and voltage V_3 which are found across resistor R_3 . From the given power dissipated, we can then solve for the possible positive values for the resistance R_3 .

EVALUATE The effective resistance feels the voltage V_{AB} across it, and the amount of current which flows through it is given by: $I_{AB} = V_{AB}/R_{123}$. This is the same current that flows through resistances R_1 and R_{23} , allowing us to write the expressions

$$I_1 = I_2 + I_3 = \frac{V_{AB}(R_2 + R_3)}{R_1(R_2 + R_3) + R_2 R_3}$$

$$V_{23} = V_{AB} - I_1 R_1 = V_{AB} \left(\frac{R_2 R_3}{R_1(R_2 + R_3) + R_2 R_3} \right)$$

Since the voltage across both R_2 and R_3 is equal to V_{23} we can express the current I_2 as $I_2 = V_{23}/R_3$, and the current I_3 as

$$I_3 = \frac{V_{AB} R_2}{R_1(R_2 + R_3) + R_2 R_3}$$

Multiplying this current by the voltage across R_3 gives the power dissipated

$$P_{23} = \left(\frac{V_{AB} R_2}{R_1(R_2 + R_3) + R_2 R_3} \right)^2 R_3$$

We are given P_{23} , V_{AB} , R_1 , and R_2 , so we can expand and simplify this expression to find the possible values of R_3 to obtain

$$C = \frac{R_3}{\alpha R_3^2 + \beta R_3 + \gamma}$$
$$R_3^2 + \left(\frac{C\beta - 1}{\alpha C} \right) R_3 + \frac{\gamma}{\alpha} = 0$$

Where

$$C = \frac{P_{23}}{V_{AB}^2 R_2^2}$$

$$\alpha = (R_1 + R_2)^2$$

$$\beta = 2R_1 R_2 (R_1 + R_2)$$

$$\gamma = R_1^2 R_2^2$$

Solving the resulting quadratic equation using the given numerical values we obtain two possible values

$$R_3 = 3.88\Omega \text{ or } 330\Omega$$

ASSESS If the current is measured, it can be used to identify which of these is the value for the unknown resistance.

- 81. INTERPRET** We will use Kirchhoff's laws to write a system of equations for the circuit shown in Fig. 25.23a, and from the resulting equations we are to determine the time constant of the circuit.

DEVELOP We first sketch our loops and nodes, as shown in the figure below. We have 3 unknowns, so we will need 3 equations. Nodes *A* and *B* give us duplicate information, so we will use only one of the two: our equations must then come from loops 1 and 2, and node *A*. Node *A* gives us

$$I_1 - I_2 - I_3 = 0$$


Loop 1 gives us

$$\mathcal{E} - I_1 R_1 - I_2 R_2 = 0$$

and loop 2 gives us

$$I_2 R_2 - V_C = 0$$

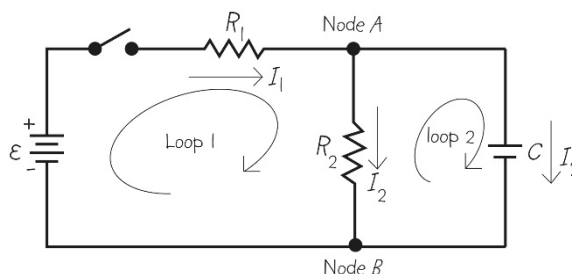The voltage across the capacitor is given by $V_C = Q/C$, and $I_3 = dQ/dt$. We will eliminate I_1 and I_2 in our system of equations, then rearrange the results into the form of Equation 25.4, from which we can easily identify the time constant.



EVALUATE From node *A*, $I_1 = I_2 + I_3$. Substitute this into the equation for loop 1:

$$\mathcal{E} - (I_2 + I_3)R_1 - I_2 R_2 = 0$$

$$I_2 = \frac{\mathcal{E} - I_3 R_1}{R_1 + R_2}$$

Now we substitute into the equation for loop 2:

$$\left(\frac{\mathcal{E} - I_3 R_1}{R_1 + R_2} \right) R_2 - V_C = 0$$

$$\mathcal{E} R_2 - I_3 R_1 R_2 = \frac{Q}{C} (R_1 + R_2)$$

We take the time derivative of this last equation:

$$-\frac{dI_3}{dt} R_1 R_2 = \frac{dQ}{dt} \frac{(R_1 + R_2)}{C}$$

$$-\frac{dI_3}{dt} R_1 R_2 = I_3 \frac{(R_1 + R_2)}{C}$$

Rearrange this slightly to obtain

$$\frac{dI_3}{dt} = -\frac{I_3}{R_1 R_2 C / (R_1 + R_2)}$$

Now here's a trick: rather than solve this equation, we note that it's the *same* equation as 25.4, with a different cluster of constants in the denominator. In the solution to 25.4, we found that $\tau = RC$, so here the time constant must be

$$\tau = \frac{R_1 R_2 C}{R_1 + R_2}$$

ASSESS This trick of putting the equation in a previously solved form can save us a lot of effort. Note that we can *only* do it because all the terms in the square brackets are constants: if there was a term involving I_3 in those brackets, then it would be a different equation and we couldn't use the same solution.

- 82. INTERPRET** We must convert a battery energy rating (in watt-hours) at a given voltage to a charge rating of ampere-hours.

DEVELOP Apply Equation 24.7, $P = IV$. The battery is specified at 50 watt-hours, which means that it can supply $P = 50 \text{ W}$ for 1 hour. We will use $P = IV$ to find I , knowing that the voltage is $V = 6 \text{ V}$.

EVALUATE $P = IV \Rightarrow I = P/V = (50 \text{ W})/(6 \text{ V}) = 8 \text{ A}$ to a single significant figure.

ASSESS This is an 8-A·h battery, which is sufficient for our requirements.

- 83. INTERPRET** This problem involves an RC circuit with a switch. We are asked to find the current supplied by the battery immediately after the switch is closed, and a long time after that.

DEVELOP Just after the switch is closed, the uncharged capacitor acts instantaneously like a short-circuit and the resistors act like two parallel pairs in series. The equivalent resistance of the combination is

$$R_{\text{eq}} = 2 \left(\frac{1}{R} + \frac{1}{2R} \right)^{-1} = \frac{4R}{3}$$

A long time after the switch is closed, the capacitor is fully charged and acts like an open circuit. Then the resistors act like two series pairs in parallel, with an effective resistance of

$$\frac{1}{R'_{\text{eq}}} = \frac{1}{R + 2R} + \frac{1}{R + 2R} = \frac{2}{3R} \Rightarrow R'_{\text{eq}} = \frac{3R}{2}$$

EVALUATE (a) Thus, immediately after the switch is closed, the current is

$$I(t=0) = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{3\mathcal{E}}{4R}$$

(b) Similarly, a long time after the switch has been closed,

$$I(t \rightarrow \infty) = \frac{\mathcal{E}}{R'_{\text{eq}}} = \frac{\mathcal{E}}{3R/2} = \frac{2\mathcal{E}}{3R}$$

ASSESS Unlike a resistor that responds instantaneously to a voltage source, a capacitors exhibits “transient” behavior. In this case, it first behaves like a short-circuit, and later an open circuit after becoming fully charged.

- 84. INTERPRET** We're asked to analyze a situation where stray voltage passes through a dairy cow.

DEVELOP The cow in this case completes the circuit. Its resistance is in series with the intrinsic resistance of the stray voltage.

EVALUATE The equivalent resistance is the sum of the cow and intrinsic resistances. The current can be found by Ohm's law:

$$I = \frac{V}{R_{\text{cow}} + R_{\text{int}}} = \frac{6 \text{ V}}{500 \Omega + 1 \text{ k}\Omega} = 4 \text{ mA}$$

The answer is (b).

ASSESS We can't say for sure what a cow feels, but this is above the threshold for sensation in humans (see Table 24.3).

85. INTERPRET We're asked to analyze a situation where stray voltage passes through a dairy cow.

DEVELOP The voltage across the cow can be found with Ohm's law.

EVALUATE Given the current from the previous problem, the voltage between the cow's tongue and hoof is

$$V_{\text{cow}} = IR_{\text{cow}} = (4 \text{ mA})(500 \Omega) = 2 \text{ V}$$

The answer is **(a)**.

ASSESS This is not a lot of voltage; it's just a little more than a D battery.

86. INTERPRET We're asked to analyze a situation where stray voltage passes through a dairy cow.

DEVELOP An ideal voltmeter is one with infinite resistance.

EVALUATE If an ideal voltmeter is attached from the water bowl to the ground, it will measure directly the emf, which in this case is 6 V.

The answer is **(c)**.

ASSESS The intrinsic resistance has no effect, since no current flows through the circuit with an ideal voltmeter.

If we chose a more realistic case, say, a voltmeter with $10 \text{ M}\Omega$ of resistance, then a tiny current will trickle through the circuit ($0.5 \mu\text{A}$), and the voltage reading will be 4.9995 V (if indeed the voltmeter's precision is this high).

87. INTERPRET We're asked to analyze a situation where stray voltage passes through a dairy cow.

DEVELOP An ideal ammeter is one with zero resistance.

EVALUATE If an ideal ammeter is attached from the water bowl to the ground, it will close the circuit and read the current as:

$$I = \frac{V}{R_{\text{int}}} = \frac{6.0 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$

The answer is **(b)**.

ASSESS This gives an idea of what the maximum current might be from the stray voltage. It also exemplifies the best way to eliminate the problem: by connecting the water bowl directly to ground. This would provide a zero-resistance pathway for current to flow, so that the cow no longer gets a shock every time it goes for a drink.